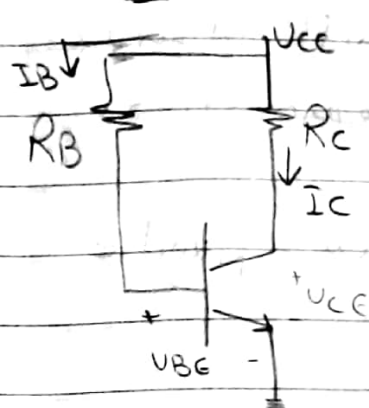


Fixed bias



$$I_C = \beta I_B$$


$$V_{CC} = R_B I_B + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

Q Point

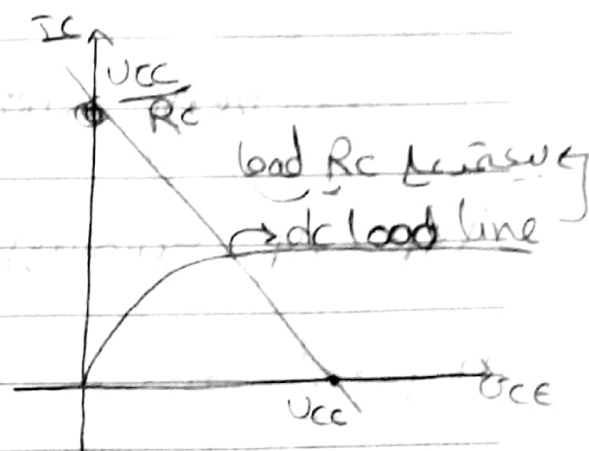


active region saturation

EX 1: find I_{BQ} , I_{CQ}

V_{CEQ} , V_B , V_C , V_{BE}

Dc

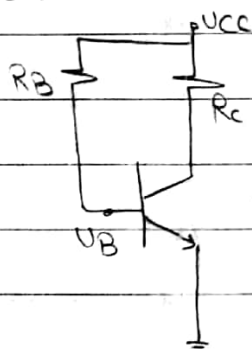

$$I_{BQ} = \frac{12 - 0.7}{240} = 47.08 \mu A$$

$$I_{CQ} = \beta I_B = 50 \times 47.08 = 2.35 \text{ mA}$$


$$V_{CEQ} = V_{CC} - I_C R_C = 12 - (2.35)(2.2) = 6.83$$

$$V_B = V_{BE} = 0.7$$

$$V_C = V_{CE} = 6.83$$

$$V_{BE} = V_B - V_C = -6.13$$
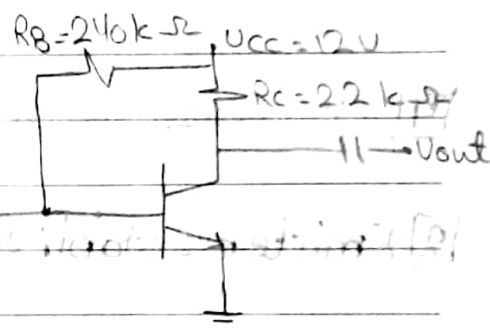
$$I_{C \text{ sat}} = \frac{V_{CC}}{R_C} = 5.45 \text{ mA}$$



2010 box 1
 ← بتغير ال β مع التغير في I_C وبالتالي هذا يترك V_{CE} ومن الممكن
 الدخول في منطقة Saturation.

fixed ← حساسيتها β very sensitive to temperature.

Type of Biasing in BJT

1] Fixed Bias circuit

2] Emitter-stabilized Bias circuit.

3] voltage divider bias.

4] Dc bias with voltage feedback.

2] Emitter-stabilized. \Rightarrow more stable.

$$I_C = \beta I_B$$


$$I_B = \alpha I_C$$

$$I_E = (\beta + 1) I_B$$

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$I_B = \frac{V_{CC} - V_{BE} - I_E R_E}{R_B}$$
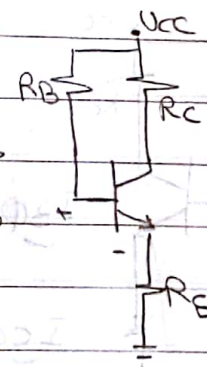
$$\textcircled{1} \uparrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$




③ Voltage divider Bias:- the best one

exact solution:-

$$R_{th} = R_1 \parallel R_2$$

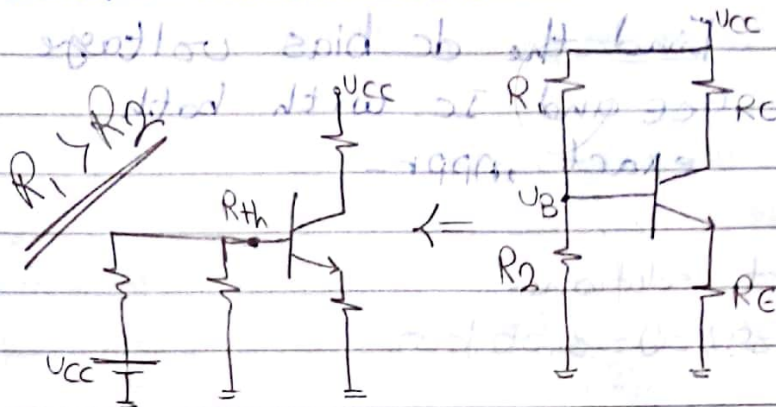
$$E_{th} = V_{cc} \times \frac{R_2}{R_1 + R_2}$$



$$I_E = (B+1) I_B$$

$$E_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$
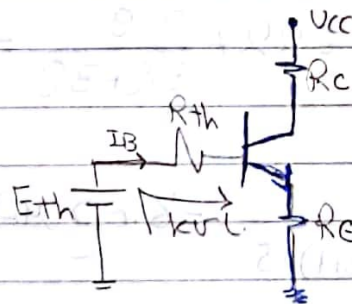
$$I_B = \frac{E_{th} - V_{BE}}{R_{th} + (B+1) R_E}$$



$$V_{ce} = V_{cc} - I_C (R_C + R_E)$$


Approximate solution:-

$$V_E = I_E R_E$$

$$R_i = \frac{V_E}{I_B} = (B+1) R_E$$

$$B \gg 1$$

$$\approx R_i = B \cdot R_E$$

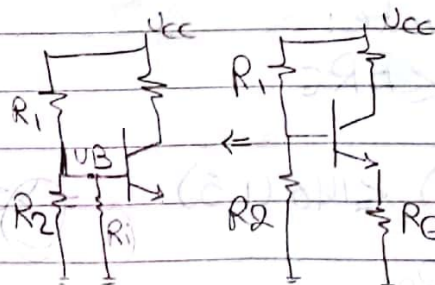


$$\approx V_B = \frac{R_2}{R_1 + R_2} V_{cc}$$

$$R_2 < R_i \Rightarrow R_i \approx \infty$$

$$10 R_2 < B R_E$$

Ex 4:-

Find the dc bias voltage V_{CE} and I_C with both exact, appr.

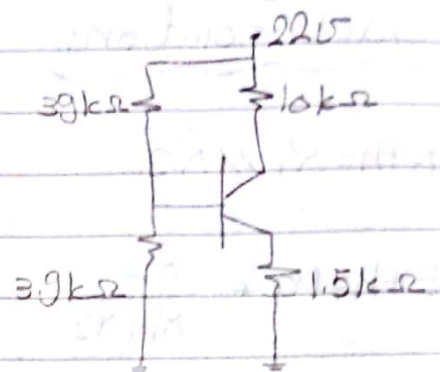 $\beta = 140$ Repeat $\beta = 70$

exact solution:-

$$R_{th} = 39 \parallel 39 = 3.55 \text{ k}\Omega$$

$$E_{th} = V_{cc} \times \frac{R_2}{R_2 + R_1} = 22 \times \frac{3.9}{3.9 + 39} = 2$$

$$I_B = \frac{2 - 0.7}{3.55 + (\beta + 1)1.5} = 6.05 \mu\text{A}$$

$$I_C = \beta I_B = 140 \times 6.05 = 0.85 \text{ mA}$$

$$V_{CE} = V_{cc} - I_C(R_C + R_E) = 12.22 \text{ V}$$

Approximate:-

$$10R_2 \leq \beta R_E$$

$$10(3.9) \leq 140(1.5) \Rightarrow \text{satisfied.}$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{cc} = 2 \text{ V}$$

$$V_E = V_B - V_{BE} = 2 - 0.7 = 1.3 \text{ V}$$

$$I_{CQ} \approx I_{EQ} = \frac{V_E}{R_E} = 0.867 \text{ mA}$$

$$V_{CEQ} = V_{cc} - I_C(R_C + R_E) = 12.03 \text{ V}$$


Frequency Response :-

تأثير التردد على شكل الإشارة و AV


Low freq
high freq

C_S, C_C, C_E

roll off
السبب في drop هو


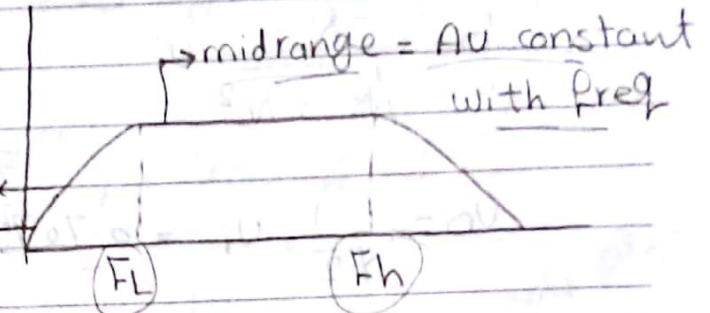


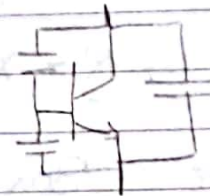كما يوجد مكشوفات داخلية تؤثر في high freq



$$X_C = \frac{1}{2\pi f C}$$

رأس كل دائرة كحصى

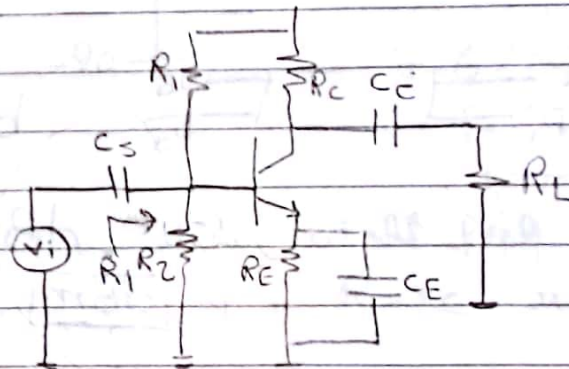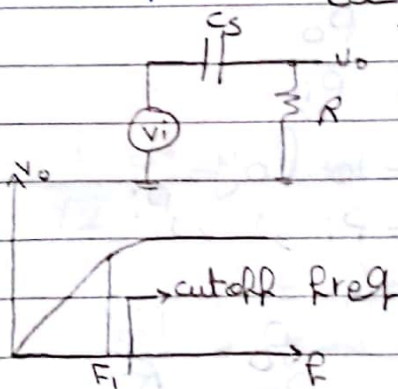

$$X_C = \frac{1}{2\pi f C} = \infty \quad \therefore f = 0$$

$$V_O = 0 \quad AV = \frac{V_O}{V_i} = 0$$

$$X_C = \frac{1}{2\pi f C} \approx 0 \quad \therefore f = \infty$$

$$\therefore V_O = V_i \quad AV = 1$$

$$V_O = V_i * \frac{R}{R - jX_C} \quad | \quad AV = \frac{R}{\sqrt{R^2 + X_C^2}} \tan^{-1} \left(\frac{X_C}{R} \right)$$

3 decimal, $V_o = \frac{1}{\sqrt{2}} V_i$ ← التردد الذي فيه يصبح F_c P_{217}


$$V_o = \frac{R}{\sqrt{R^2 + X_c^2}} V_i \quad \underline{R = X_c}$$

$$V_o = \frac{1}{\sqrt{2}} V_i = 0.707 V_i \quad V_o = 70\% V_i \quad \left. \begin{array}{l} \text{cutoff Freq} \end{array} \right\}$$

$$P_{out} = \frac{1}{2} P_{in}$$

$$\text{At } R_1 \Rightarrow R = X_c = R = \frac{1}{2\pi f C} \quad F_1 = \frac{1}{2\pi R C}$$

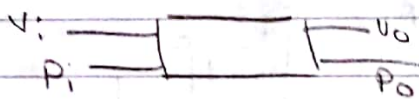Band width \rightarrow C كبيرة \rightarrow Δf كبير



$$\text{bel} = \log_{10} \frac{P_o}{P_i}$$

$$\text{dB} = \text{Decibel} = 10 \log \frac{P_o}{P_i} \quad \text{لو } P_i = 1 \text{ mW} \text{ فتمسك } [dBm]$$

$$A_p = 10 \log \frac{P_o}{P_i}$$

$$P_o = \frac{V_o^2}{R}$$

$$A_v = 20 \log \frac{V_o}{V_i}$$

$$\frac{V_o}{V_i} = \frac{R}{\sqrt{R^2 + X_c^2}} \tan^{-1} \frac{X_c}{R} = \frac{1}{\sqrt{1 + (\frac{X_c}{R})^2}} \tan\left(\frac{X_c}{R}\right)$$

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + (\frac{F_1}{F})^2}} \tan^{-1} \frac{F_1}{F}$$

Write

$$\text{at } f \ll R_1 \text{ , } i \left(\frac{R_1}{F} \right) \gg 1$$

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{F_1}{F} \right)^2}} \tan^{-1} \left(\frac{R_1}{R} \right) = 20 \log \frac{1}{\sqrt{1 + \left(\frac{F_1}{F} \right)^2}} \quad \text{في } \frac{1}{\sqrt{2}}$$

$$A_{v_{dB}} = -10 \log \left(1 + \left(\frac{F_1}{F} \right)^2 \right) = -20 \log \frac{F_1}{F}$$

$$\text{At } F = F_1$$


$$\frac{F_1}{F} = 1$$

$$-20 \log 2 = 0 \text{ dB}$$

$$\text{At } F = \frac{F_1}{2}$$

$$\frac{F_1}{F} = 2$$


$$-20 \log 2 = -6 \text{ dB}$$

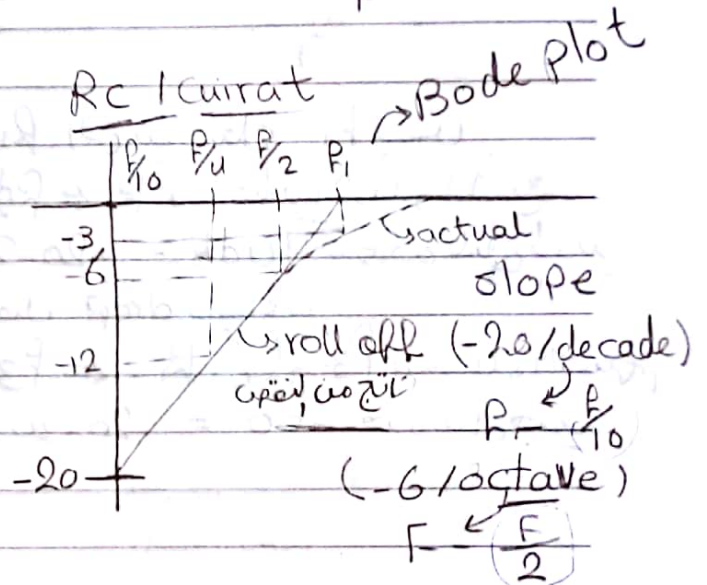

$$A_v = \frac{1}{\sqrt{2}} \Rightarrow -3 \text{ dB} \text{ drop at cutoff freq. } \leftarrow$$

$$V_o = \frac{1}{\sqrt{2}} V_i \text{ و } R = X_C \text{ و}$$
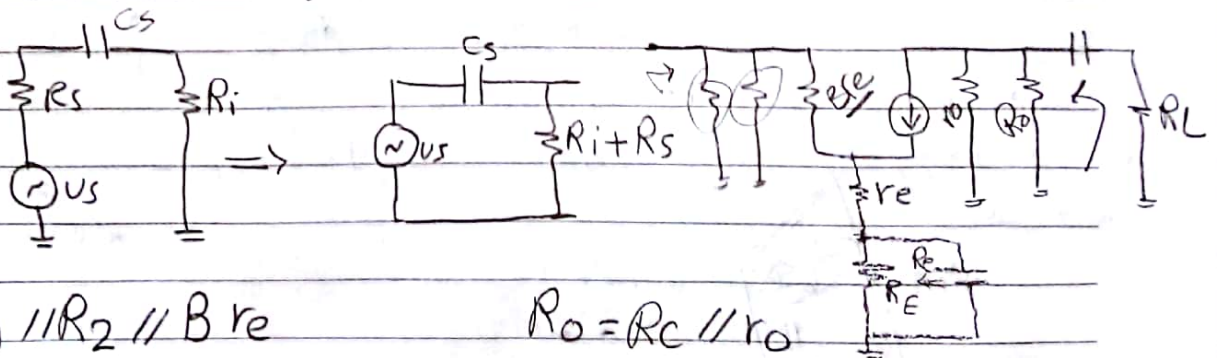
$$A_v = -20 \log \frac{1}{\sqrt{2}} = +3$$



$$R_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$R_o = R_C \parallel r_o$$


$$F_1 = \frac{1}{2\pi C (R_i + R_s)}$$

$$F_2 = \frac{1}{2\pi C (R_L \parallel R_o)}$$

$$R_e = R_E \parallel \left(r_e + \frac{R_1 \parallel R_2 \parallel R_3}{\beta} \right)$$

$$F_3 = \frac{1}{2\pi C R_e}$$

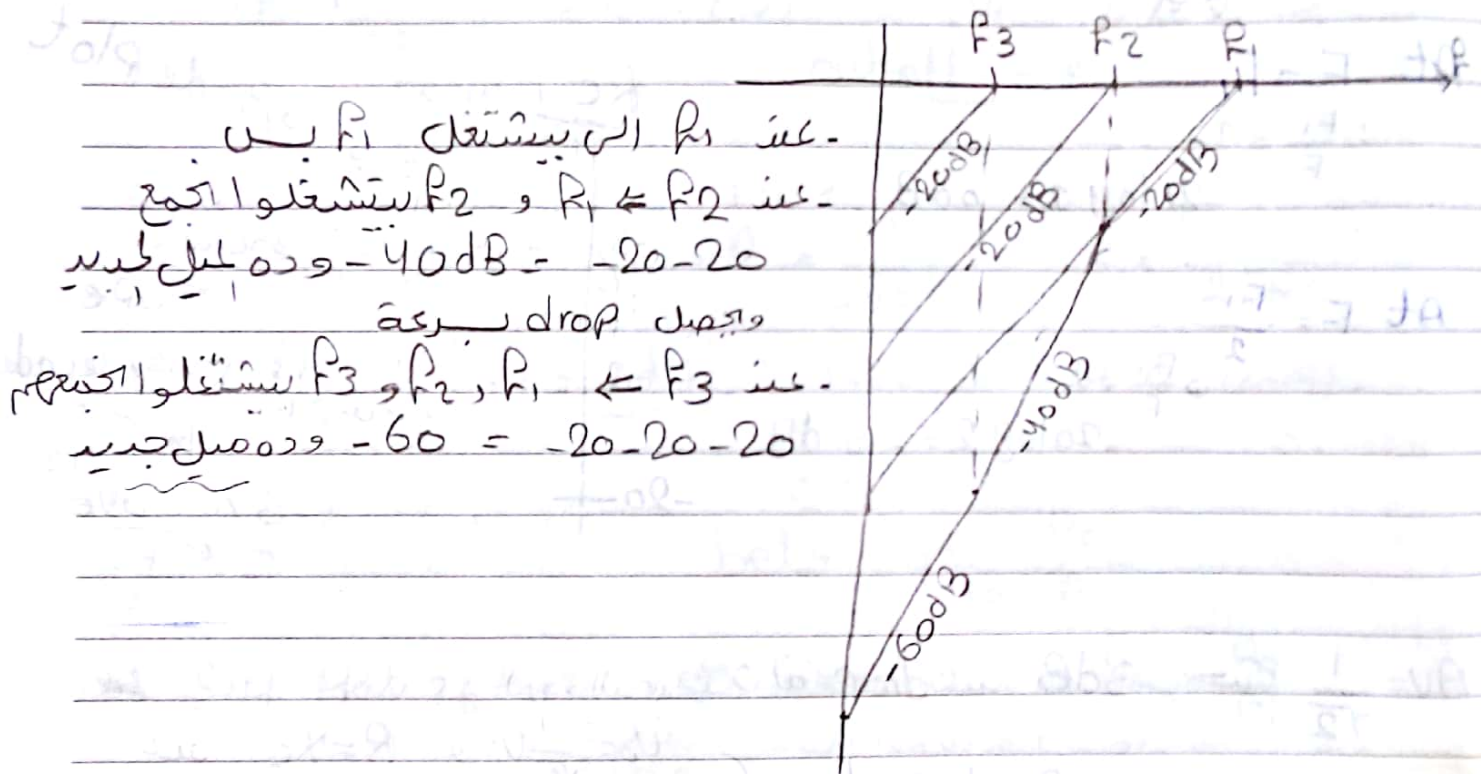التردد الذي يربط drop أكبر
بيترسوا بنفس الميل -20dB/decade



Low Frequency Response BJT and FET

Dc analysis

V.S \rightarrow S.C

C.S \rightarrow O.C

|| \rightarrow O.C

$\infty \rightarrow$ S.C $X_C = \infty$

$\leftarrow V_{CE}, I_C, I_D$

Ac analysis



① V.S \rightarrow S.C

C.S \rightarrow O.C

|| \rightarrow S.C



$\infty \rightarrow$ O.C

② model

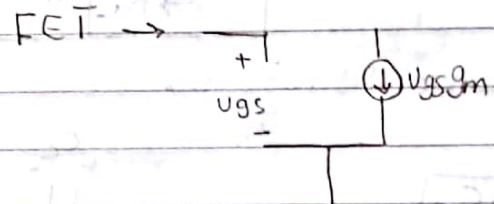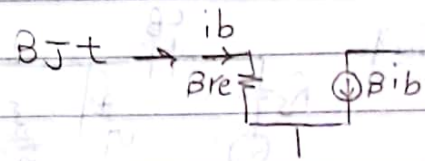

R_{in}, R_{out}, A_v

Frequency Response

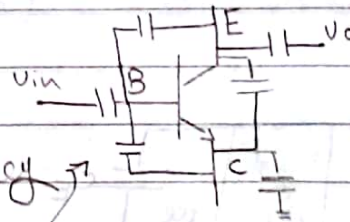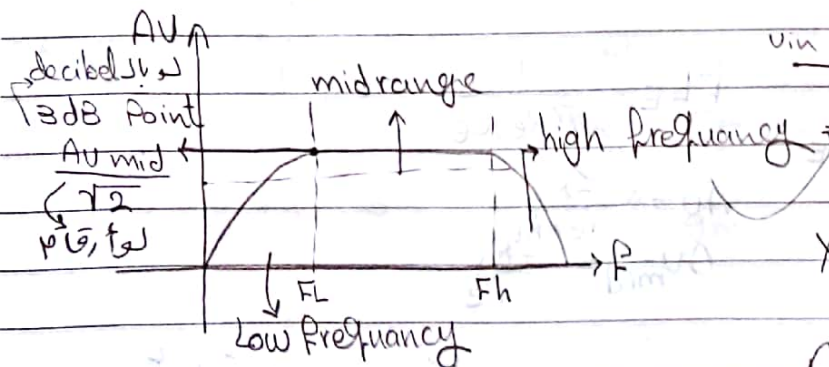



$$X_C = \frac{1}{2\pi f C} \quad \leftarrow \text{تغییر } f \text{ تغییر } X_C \text{ تغییر } A_v$$

$$A_v = f(R_C, X_C)$$

Q9


Write

Low frequency BJT

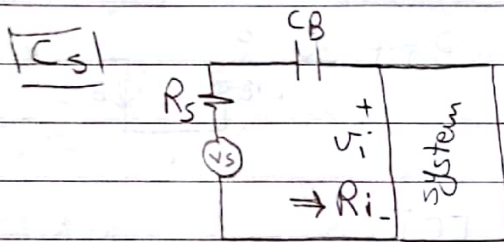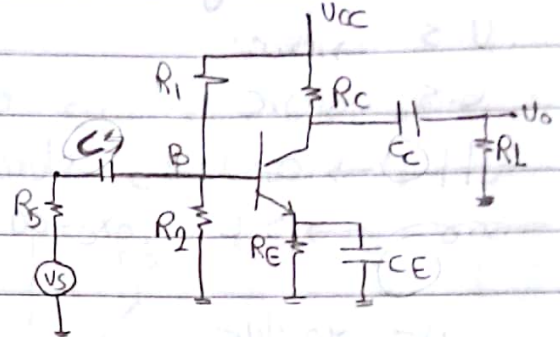


$$P_{LB} = \frac{1}{2\pi(R_S + R_i)C_B}$$
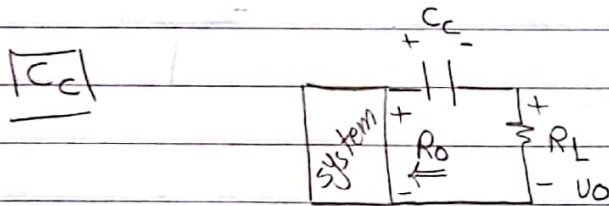
$$A_{U_{mid}} = V_O \times \frac{R_i}{R_i + R_S} \quad C_B \rightarrow S.C$$



$$P_{LC} = \frac{1}{2\pi(R_L + R_O)C_C}$$


$R_O \rightarrow$ AC Analysis

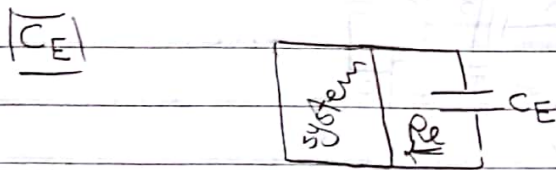

$$P_{LE} = \frac{1}{2\pi(r_e)C_E}$$

$$A_U = \frac{-R_C}{r_e \parallel R_E}$$

$$A_{U_{mid}} = \frac{-R_C}{r_e}$$

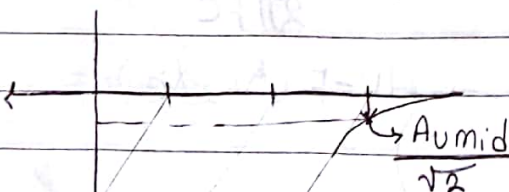

$$F_L = \omega_L \times \frac{1}{\sqrt{2}}$$

M1 FET

$$F_{LG} = \frac{1}{2\pi(R_{\text{signal}} + R_i)C_G}$$

$$F_{LD} = \frac{1}{2\pi(R_o + R_L)C_D}$$

$$P_{LS} = \frac{1}{2\pi R_{eq} C_S}$$

$$F_{ET} \approx 1 + \frac{1}{\omega C_S R_{eq}}$$



$$I) g_{mo} = \frac{2I_{DSS}}{V_P}$$

$$g_m = g_{mo} \left[1 - \frac{V_{GS}}{V_P} \right]$$

$$I_{DSS} = I_S \quad \left\{ \begin{array}{l} \text{at } V_{GS} = 0 \\ V_{th} = V_P \end{array} \right.$$

$$II) I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2 \quad \text{--- (1)}$$

13) a) Bypassing μ of Q_1 (dB) I_{DQ} , V_{GSQ}

$$R_{eq} = \begin{matrix} r_d \neq \infty & R_S \\ 1 + R_S [1 + g_m r_d] / [r_d + (R_D \parallel R_L)] \end{matrix}$$

$$r_d = \infty \quad R_S \parallel \frac{1}{g_m}$$

9.7

14 with early effect $r_o = 40 \text{ k}\Omega$

15 19

16 20

17 21 report



18 22

23, 24, 25 report

15

$$r_e = \frac{U_{th} \leftarrow 26 \text{ mV}}{I_E \leftarrow \text{DC analysis}}$$

DC Analysis

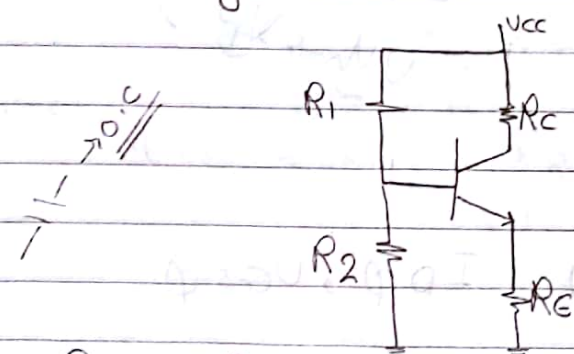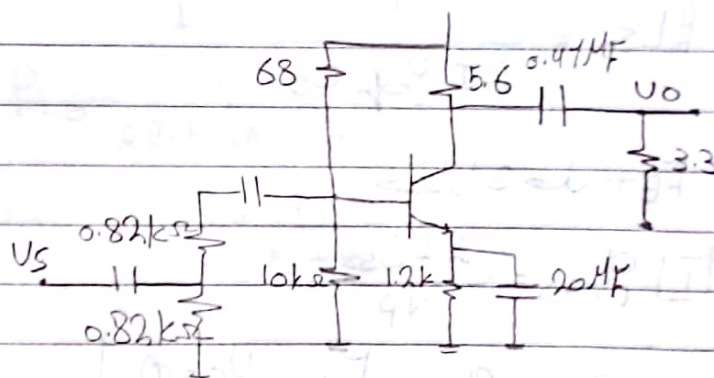

$$10R_2 \leq B R_E$$

$$10 \times 10 \text{ k}\Omega \leq 120 \times 1.2 \text{ k}\Omega$$

$$100 \text{ k}\Omega \leq 144 \text{ k}\Omega$$


$$V_B = V_{CC} \times \frac{R_2}{R_1 + R_2} = 14 \times \frac{10 \text{ k}}{10 \text{ k} + 68 \text{ k}} = 1.794 \text{ V}$$

$$V_{BE} = V_B - V_E \quad \text{where } V_E = 0.7 \text{ V} \quad \Rightarrow V_{BE} = 1.79 - 0.7 = 1.095 \text{ V}$$

$$I_E = \frac{V_{BE}}{R_E} = 0.913 \text{ mA}$$

$$\therefore r_e = \frac{26 \text{ mV}}{0.913 \text{ mA}} = 28.46 \Omega$$

2] AC Analysis

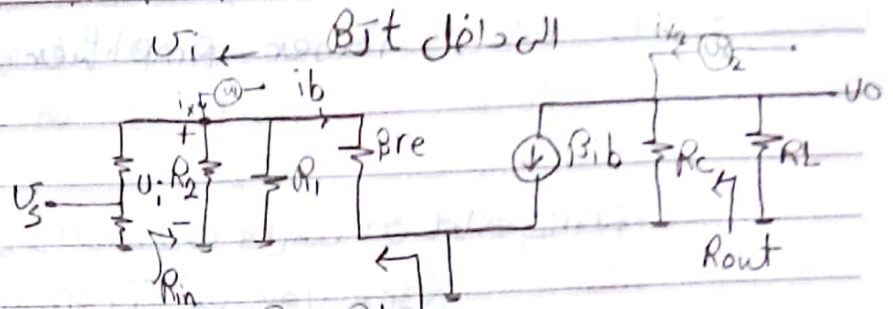


$$A_{v_{mid}} = \frac{V_o}{V_i} = \frac{-\beta i_b (R_C \parallel R_L)}{\beta i_b r_{be}} = \frac{-R_C \parallel R_L}{r_{be}}$$

$$Z_i = \frac{V_x}{i_x} = R_1 \parallel R_2 \parallel \beta r_{be}$$

$$Z_{out} = \frac{V_{x2}}{i_{x2}} = R_C$$

$$A_{v_s} = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_i} \times \frac{V_i}{V_s}$$

over all gain

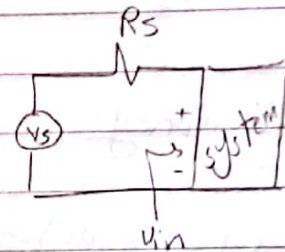

$$V_i = V_s \times \frac{Z_{in}}{R_s + Z_{in}}$$

$$A_{v_s} = \frac{-R_C \parallel R_L}{r_{be}} \times \frac{Z_{in}}{R_s + Z_{in}}$$


$R_s \leftarrow$ المقاومة

$$F_{LB} = \frac{1}{2\pi C_B (Z_i + R_s)} = 103.4$$

$$F_{LE} = \frac{1}{2\pi C_E (20 + R_C)} = 38.05$$

$$F_{HE} = \frac{1}{2\pi C_E (R_E)} = 749.51$$

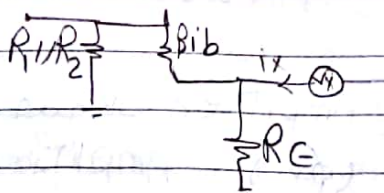لأعلى
منخفضة لقيمة B ينزل
منخفضة لقيمة B يرفع
خرج \$R_C\$ و \$R_E\$ و \$R_C\$



$$R_{out} = \frac{V_x}{i_x} = R_E \parallel \frac{\beta r_{be} + R_1 \parallel R_2}{\beta}$$

$$F_L = F_{LE} = 749.51$$

Power Amplifier

large signal → power

تكنولوجيا C, E, B بين وجود الفقد في كل من الـ A و B

Receiver و Transmitter




في تصميم Amplifier في A و B

1- efficiency

$$\text{Efficiency} = \frac{P_o(\text{dc})}{P_i(\text{dc})} \%$$

$$P_o(\text{dc}) = I_{L(\text{rms})}^2 R_L$$

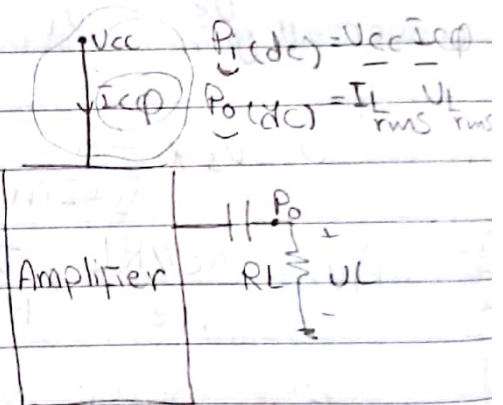
$$P_o(\text{dc}) = \frac{V_{L(\text{rms})}^2}{R_L}$$



In practice $\neq 100\%$
because of

1- heat dissipation in the transistor

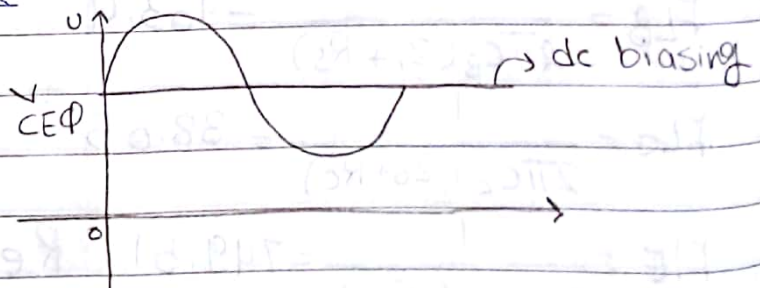2- matching of impedance between Load and output of amplifier



buffer $\sin P$ high, out P low, gain = 2

في تصميم Amplifier على أساس فترة وجود التيار أي أن يكون





(on) Amplifier



Amplifier classes represent the amount of the output signal varies over one cycle of operation for a full cycle of input

class A


class B (push pull)

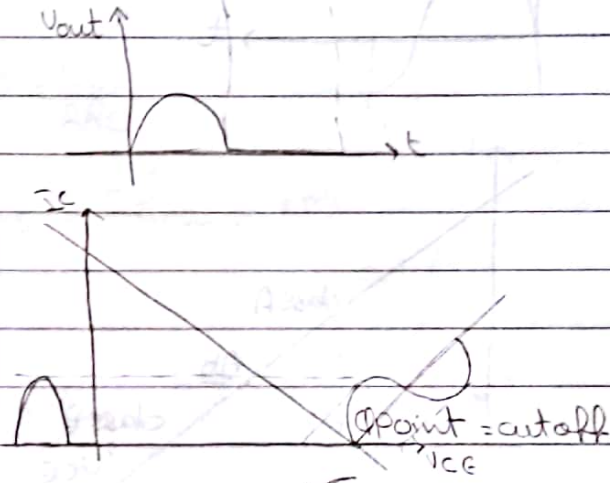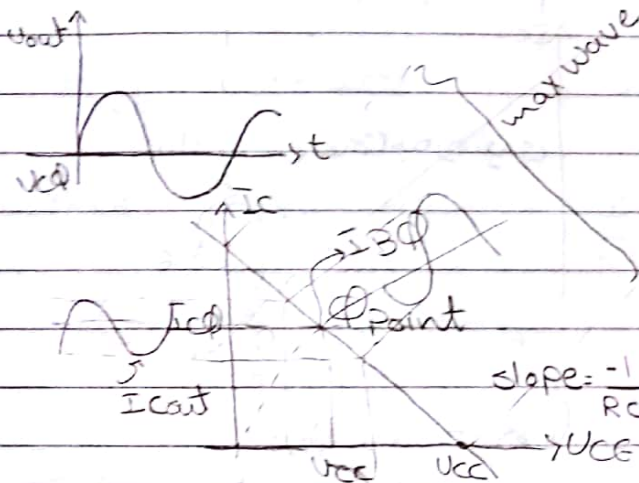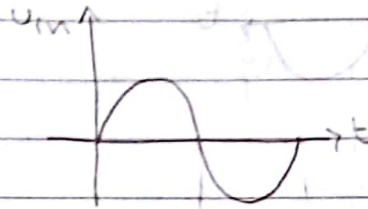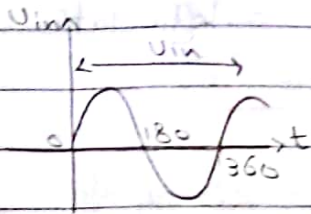

أقل كفاءة، وذلك يعود ودرجة التباين، وبذلك يكون أقل كفاءة

هذه الكفاءة ولكن ليس بالكفاءة المطلوبة حيث التباين، الموجود في الفترة فقط

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

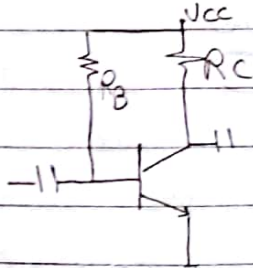

$$I_B = \frac{V_{CC} - 0.7}{R_B}$$

180°

48%

والتباين في V_{CE} هو $\frac{V_{CC}}{2}$ والتباين في I_C هو $\frac{I_{CQ}}{2}$ max wave



360° ← operating cycle
25% to 50% ← efficiency

class A \rightarrow class B \rightarrow class AB \rightarrow class C

efficiency \nearrow زیادہ

Date _____ Subject _____



class AB

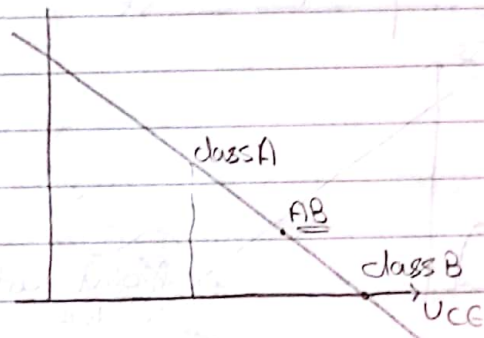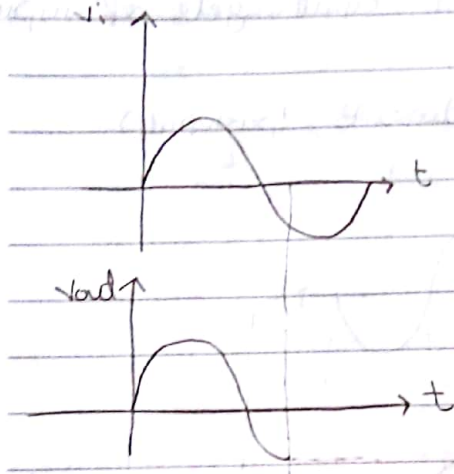

180° to 360°

From 50% to 78.5

class C

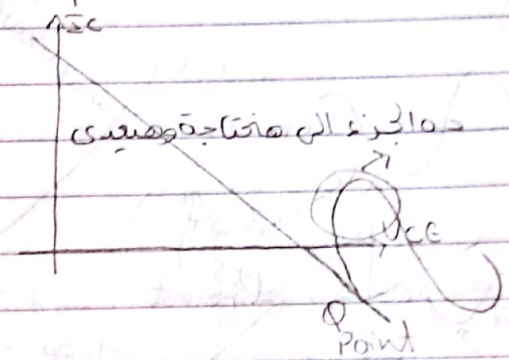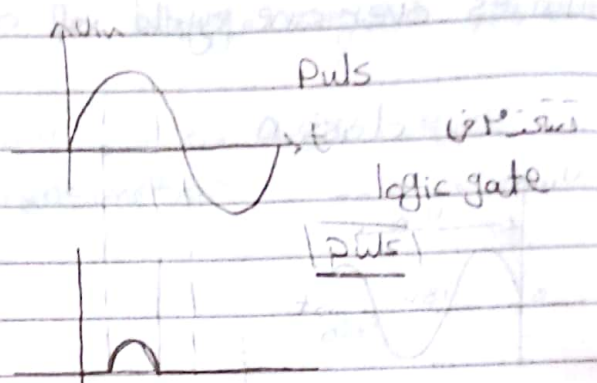

less than 180°
not used for delivering
large amount of power
thus the efficiency is not
given

class A

$$I_B = \frac{V_{CC} - 0.7}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$\text{efficiency} = \frac{P_o(\text{dc})}{P_i(\text{dc})}$$

$$P_i(\text{dc}) = V_{CC} I_{CP}$$

$$I_{CP} = \frac{V_{CC}}{2R_C}$$

$$V_{\text{rms}} = \frac{V_P}{\sqrt{2}}$$

$$P_o(\text{dc}) = V_{\text{CErms}} I_{\text{C rms}} = \frac{V_{\text{CErms}}^2}{R_C} = I_{\text{C rms}}^2 R_C$$

maximum efficiency

$$V_{P \text{ top}} = V_{CC}$$

$$I_{P \text{ top}} = \frac{V_{CC}}{R_C}$$

max swing

$$P_o = \frac{V_{CC}^2}{8R_C}$$

$$\frac{V_{CC}}{2\sqrt{2}} \cdot \frac{V_{CC}}{2\sqrt{2} R_C} = \frac{V_{CC}^2}{8R_C} = P_o(\text{dc})$$

correctly depend on I_C
eff ↓

$$\text{efficiency} = 25\%$$

ex:- $V_{CC} = 20V$ $R_C = 20\Omega$ $R_B = 1k\Omega$ $\beta = 25$

Base current 10 mA Peak

$$P_i(\text{dc}), P_o(\text{dc}), \eta$$

$$P_o = \frac{I_{CP}^2}{2} R_C = 0.625W$$

$$I_{BQ} = \frac{20 - 0.7}{1} = 19.3 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 25(19.3) \approx 0.48A$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 10.4V$$

$$I_{CP} = \frac{25}{\beta} \times \frac{10}{I_B} = 0.25 \text{ (peak)}$$

$$P_i = \frac{V_{CC}(I_{CP})}{2} = 9.6$$

$$\eta = 6.5\%$$

Write

class ~~BA~~ Aclass A ~~LC~~ circuittransformer coupled
class A Amplifier.Wilson Transformer ~~LC~~ RC circuit
matching circuit


transformer

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$

$$\frac{R_L}{R_L'} = \frac{V_2/I_2}{V_1/I_1} = \frac{V_2 I_1}{V_1 I_2} = \frac{N_2 N_2}{N_1 N_1} = \left(\frac{N_2}{N_1}\right)^2$$

$$\frac{R_L'}{R_L} = \left(\frac{N_1}{N_2}\right)^2 = d^2$$

$$(R_L') = d^2 R_L \leftarrow \text{effective resistance.}$$

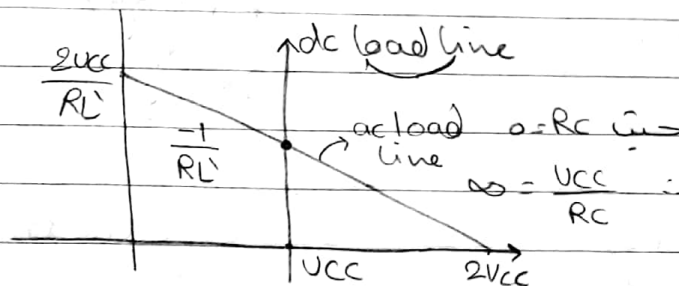S.C \leftarrow transformer DC is50% \leftarrow accuracy of design



$$V_{ce(p-p)} = 2V_{cc}$$

$$I_{c(p-p)} = \frac{2V_{cc}}{R_L}$$


$$P_{i(dc)} = V_{cc} I_{c(p-p)} = V_{cc} \times \frac{V_{cc}}{R_L'} = \frac{V_{cc}^2}{R_L'}$$

$$P_{o(dc)} = \frac{V_{ce(p-p)} I_{c(p-p)}}{8} = \frac{V_{cc}^2}{2R_L'} \quad \frac{V_{cc}}{\sqrt{2}} \cdot \frac{V_{cc}}{R_L/\sqrt{2}}$$

$$\eta = 50\%$$

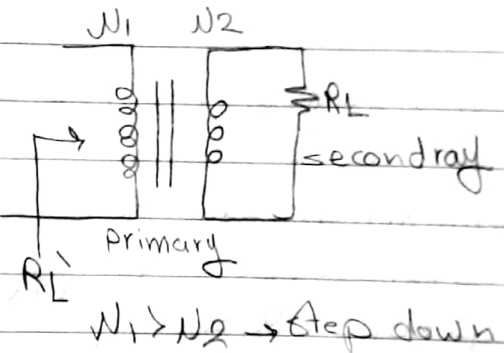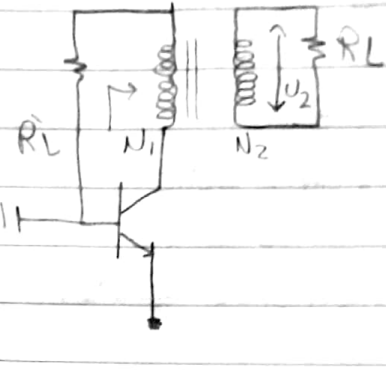

dc load line

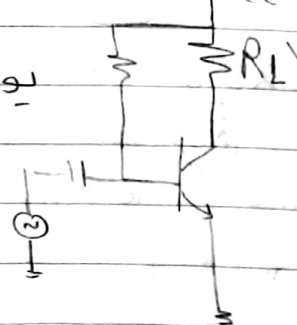

Write

1.6 Find PL



I dc analysis

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$20 - I_B 470 - 0.7 + (B+1) I_B R_E = 0$$

$$I_B = 33.8 \mu A$$

$$I_E = (B+1) I_B = 3.752 \text{ mA}$$

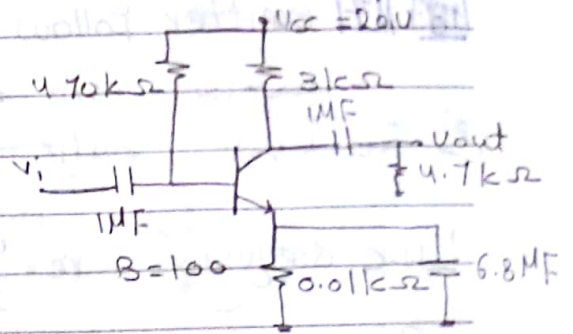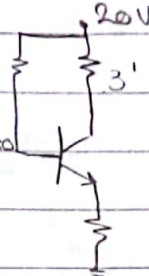


$$r_e = \frac{V_T}{I_E} = 6.93 \Omega$$

II ac analysis

$$R_{in} = R_B \parallel B r_e$$

$$A_v = \frac{-B r_e (R_C \parallel R_L)}{r_e} = \frac{-R_L \parallel R_C}{r_e}$$

$$R_o = R_C$$

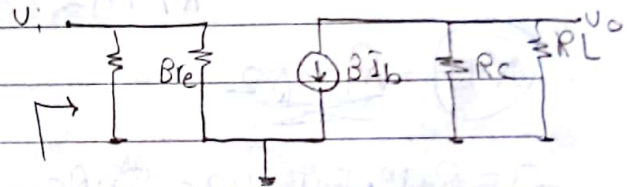


$$R_{eq} = \frac{R_E \parallel (B r_e + R_B)}{(B)}$$

$$F_{LB} = \frac{1}{2\pi(R_S + R_i)C_S} = 116.93 \text{ Hz}$$

$$F_{LC} = \frac{1}{2\pi(R_o + R_L)C_C} = 20.67 \text{ Hz}$$
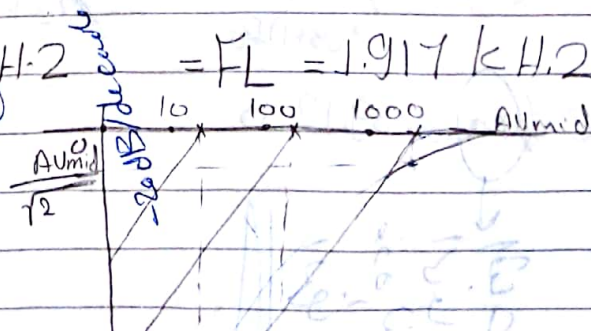
$$F_{LE} = \frac{1}{2\pi(R_{eq})C_E} = 1.917 \text{ kHz} = F_L = 1.917 \text{ kHz}$$



Unit

181 17 emitter follow = collector

[3] $\rightarrow FLB$ in/P = 71.92 H.2
 $\rightarrow FL$ $\rightarrow xlc$ out/P = 193.16 H2 = FL

II Oc analysis $r_e = \frac{V_{th}}{I_E}$

$BRE \gg 10R_2$




$100 \times 2.2 \gg 10 \times 30$

$22k \gg 300k$ Not satisfied


$E_{th} = V_B = V_{cc} \times \frac{R_2}{R_1 + R_2}$

$R_{th} = R_1 \parallel R_2$

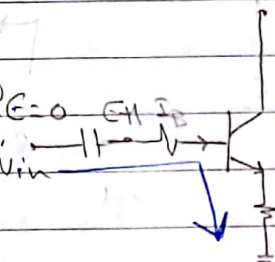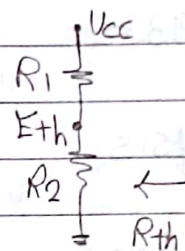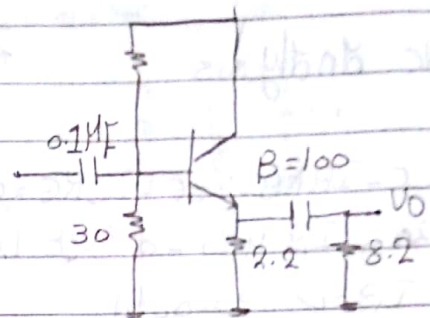$-I_B R_{th} + E_{th} - V_{BE} - I_E R_E = 0$
 $I_B = 8.53 nA$
 $I_E = 0.86 mA$
 $r_e = 30.2 \Omega$



12 Ac analysis

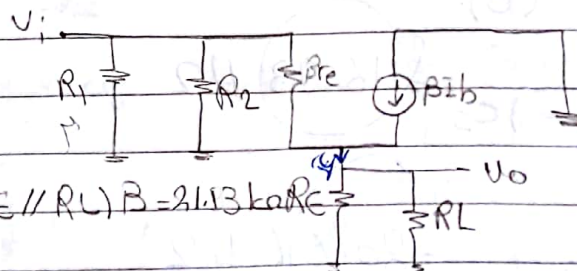

$R_{in} = R_1 \parallel R_2 \parallel \beta r_e + (R_E \parallel R_L) \beta = 21.13 k\Omega$

$A_v = \frac{V_o}{V_i} = \frac{(R_E \parallel R_L)}{\beta r_e + (R_E \parallel R_L)} = \frac{(R_E \parallel R_L)}{r_e + (R_E \parallel R_L)} = 0.983$

$R_o = R_E \parallel r_e = 39.12 \Omega$

Write

Q31

DC analysis

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$



6mA $V_P = -6$

Biasing

$$0 - V_{GS} - I_D R_S = 0$$

$$V_{GS} = -I_D R_S$$

$1.2\text{k}\Omega$

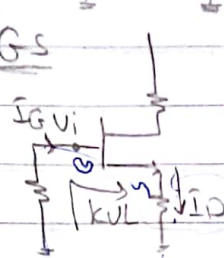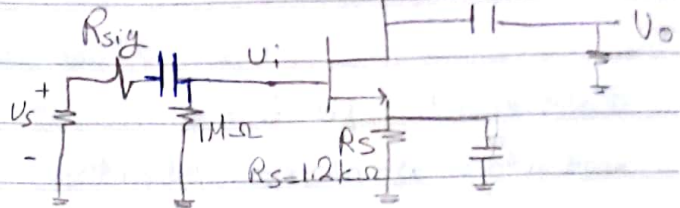

$$g_{mo} = \frac{2I_{DSS}}{|V_P|} = \frac{2 \times 6 \times 10^{-3}}{6} = 2\text{mS}$$

$$V_{GS} = -2.45$$

$$I_D = 2.1\text{mA}$$


$$g_m = g_{mo} \left[1 - \frac{V_{GS}}{V_P} \right] = 1.18\text{mS}$$

$$R_{in} = R_G \parallel \infty = R_G$$

$$A_v = \frac{-g_m V_{GS} (R_D \parallel R_L)}{V_{GS}} = -g_m (R_D \parallel R_L)$$

$$R_{out} = R_D$$
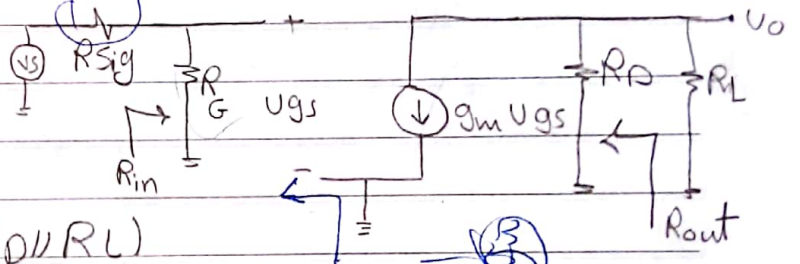
$$R_{eff} \leftarrow \text{source impedance} = \frac{1}{g_m} \parallel R_S$$



19:30


I_{DSS}

Write


millier effect capacitance

for inverting amplifier (phase shift = 180°)


input and output capacitance increased by capacitance level sensitive To inter electrode capacitance between input and output. Terminals.

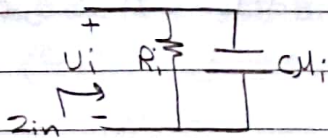 C_{Mi} 

$$C_{Mi} = (1 - A_V) C_F$$

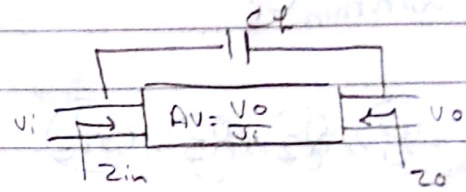


$$C_{Mi} = (1 - A_V) C_F$$

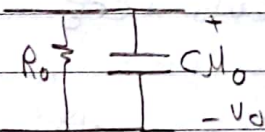 C_{Mo} 

$$C_{Mo} = (1 - \frac{1}{A_V}) C_F$$

$$C_{Mo} = (1 - \frac{1}{A_V}) C_F$$


S.C. external and internal capacitance

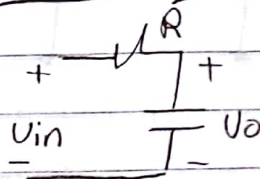High pass Filter

$$\frac{1}{\omega R C} = 1$$

$$\frac{1}{\omega R C} = 1$$

121

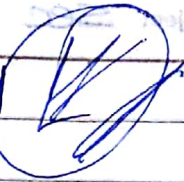

115,161

mod-8

$n \rightarrow 10$
 -12

$P \rightarrow 10$
 -15

$F \rightarrow 10$
 -15

$r_e = 28.46 \Omega$

$A_v = -72.91$

$F_{H_i} = \frac{1}{2\pi R_{th_i} C_i}$

$F_{H_o} = \frac{1}{2\pi R_{th_o} C_o}$

$R_{th_i} = R_1 \parallel R_2 \parallel R_s \parallel \beta r_e$

$R_{th_o} = R_L \parallel R_C \parallel r_o =$

$C_i = C_{M_i} + C_{W_i} + C_{B_E} = (1 - A_v) C_{B_E} + C_{W_i} + C_{B_E}$


$C_o = C_{M_o} + C_{W_o} + C_{C_E} = (1 - \frac{1}{A_v}) C_{B_E} + C_{W_o} + C_{C_E}$

31

model

$R_{th_i} = R_{s_i} \parallel R_{G_2}$

$R_{th_o} = R_L \parallel R_D$

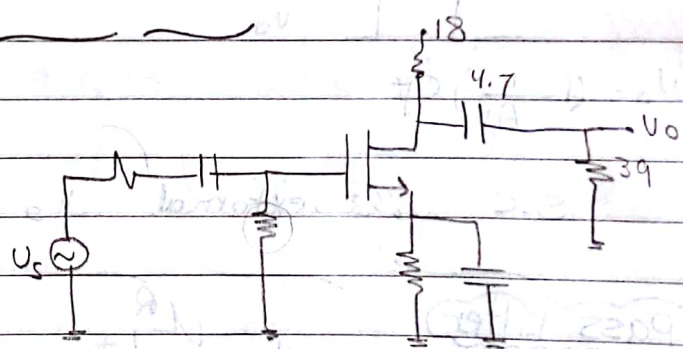

$C_i = C_{W_i} + C_{G_E} + (1 - A_v) C_{G_D}$

$C_o = C_{W_o} + C_{D_S} + (1 - \frac{1}{A_v}) C_{G_D}$

$A_v = -2$

$g_m = 1.78 \text{ m}\Omega^{-1}$

$F_{H_i} = \frac{1}{2\pi C_i R_{th_i}}$

$F_{H_o} = \frac{1}{2\pi C_o R_{th_o}}$

Write

when $\eta = 50\%$

← max efficiency

$$\eta = 50 \left[\frac{V_{CEmax} - V_{CEmin}}{V_{CEmax} + V_{CEmin}} \right]^2 \%$$

$V_{CEQ} + V_P$

$V_{CEQ} - V_P$



Class B



→ $I_B = 0$ in Biasing circuit

(Puls) → distortion due to

distortion due to

C.E. inverting circuit

$V_i = V_{out}$

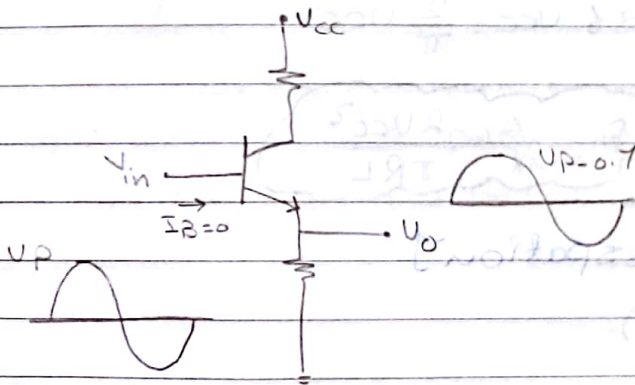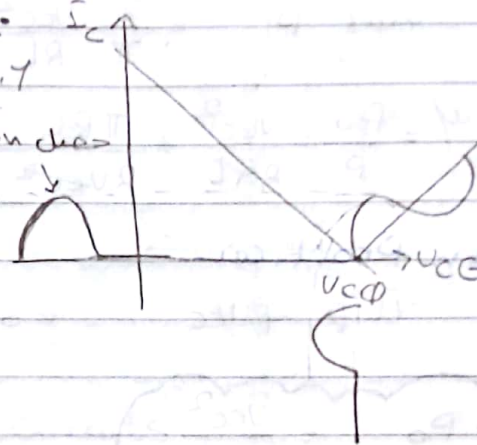

$$\eta = \frac{P_o(d.c)}{P_i(d.c)}$$


$$I_{Ldc} = \frac{2}{\pi} I_P$$

$$P_{in} = V_{CC} \times I_{CQ}$$

$$P_{in} = V_{CC} \times \frac{2 I_P}{\pi}$$

$$P_o = \frac{V_{L(rms)}^2}{R_L} = \frac{V_{L(p.p)}^2}{8 R_L} = \frac{V_{LP}^2}{2 R_L}$$
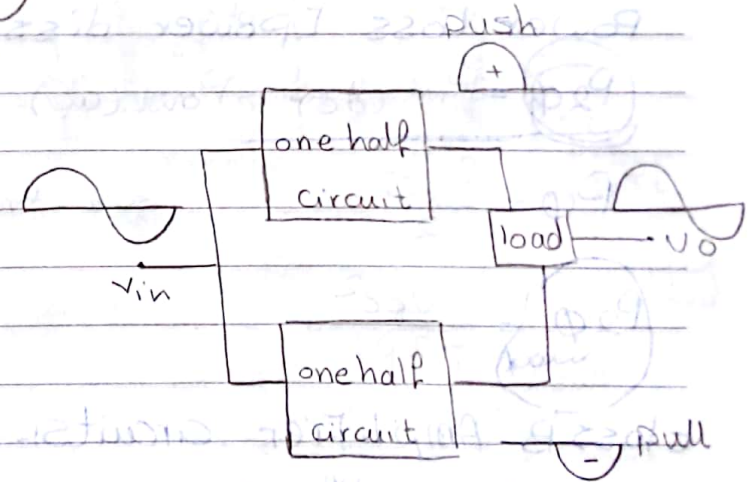
$$\eta = \frac{V_{LP}^2}{2 R_L \times 2 I_P V_{CC}} \times \frac{\pi}{4} = \frac{\pi}{4} \frac{V_{LP}}{V_{CC}} \times 100\%$$



class B = Push-pull amplifier

Write

→ max power consideration:-

$$\max P_{out} \Big|_{V_{LP} = V_{CC}} = \frac{V_{CC}^2}{2R_L}$$

$$I_{dc} = \frac{2}{\pi} I_P = \frac{2}{\pi} \cdot \frac{V_{CC}}{R_L}$$

$$\max P_i = \frac{2}{\pi} \frac{V_{CC}^2}{R_L}$$

$$\eta = \frac{P_o}{P_i} = \frac{V_{CC}^2}{2R_L} \times \frac{\pi R_L}{2V_{CC}^2} = \frac{\pi}{4} \times 100 = 78.53\%$$

In Practice:-

$$V_{LP} \neq V_{CC} = 0.636 V_{CC} = \frac{2}{\pi} V_{CC}$$

$$P_{o \max} = \frac{V_{CC}^2}{2R_L}$$

$$P_{i \max} = \frac{2V_{CC}^2}{\pi R_L}$$

Power loss [power dissipation]

$$P_{2\phi} = P_{in}(dc) - P_{out}(ac)$$


$$P_{\phi} = \frac{P_{2\phi}}{2} \leftarrow \text{one transistor.}$$

$$P_{2\phi \max} = \frac{2V_{CC}^2}{\pi^2 R_L}$$



class B Amplifier circuits:-

→ phase splitters


لوازم استلزام (pnp, npn) 2φ

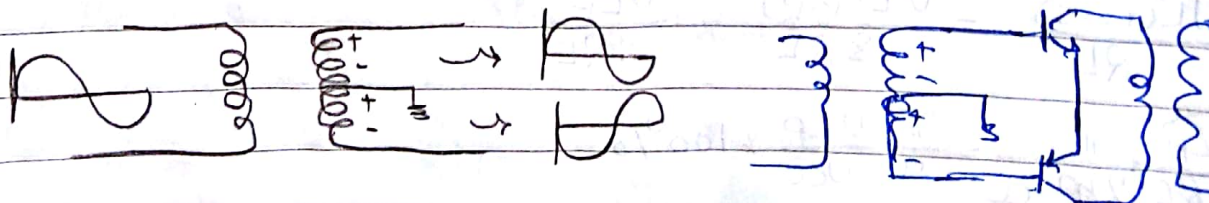

1 Complementary symmetry circuit

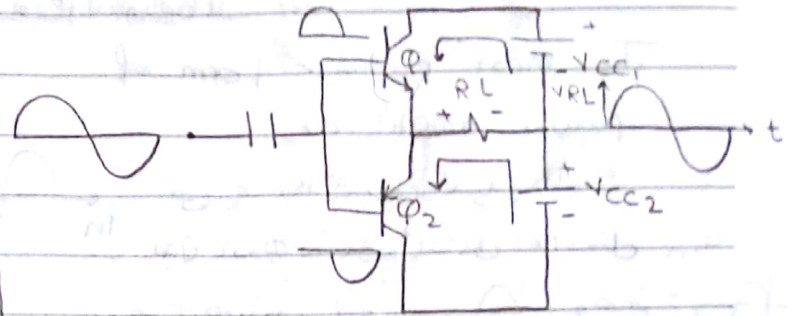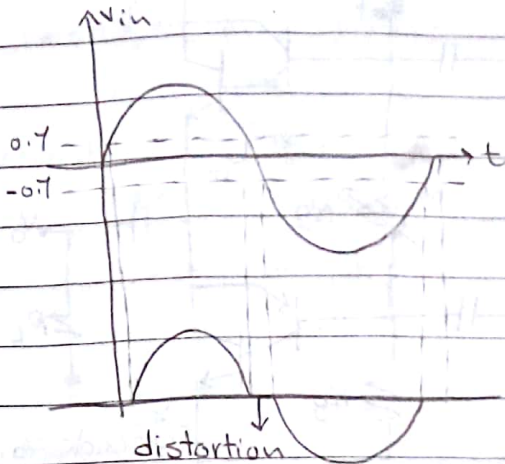


Class AB Biasing circuit

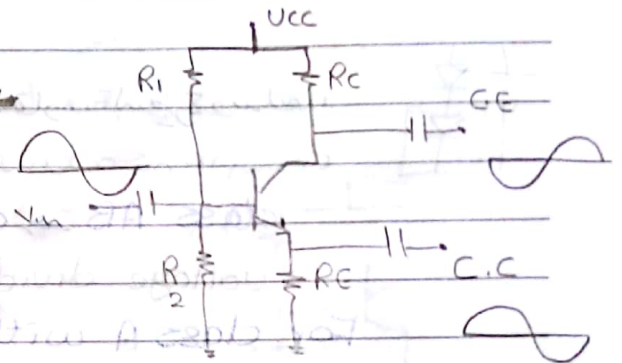

2 Transform-coupled push pull circuits

matching $\omega_{in} = \omega_{out}$

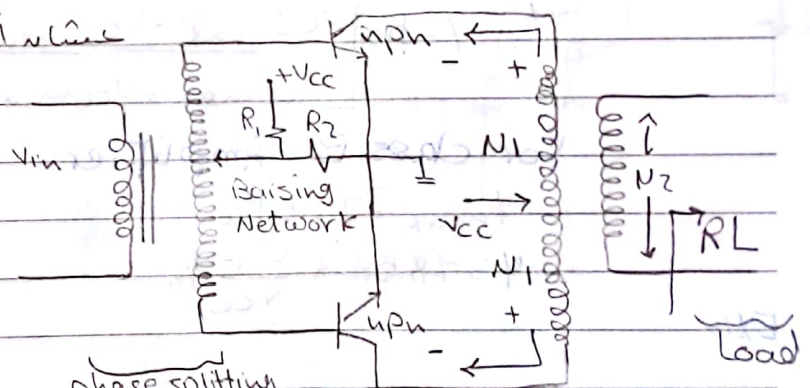

phase splitting input transformer

push pull circuit connection

push pull output transformer

$$B_T = B_1 B_2$$


complementary

high current gain

out impedance \downarrow

$P_{in} \approx P_{out}$

$P_{in} \approx P_{out}$

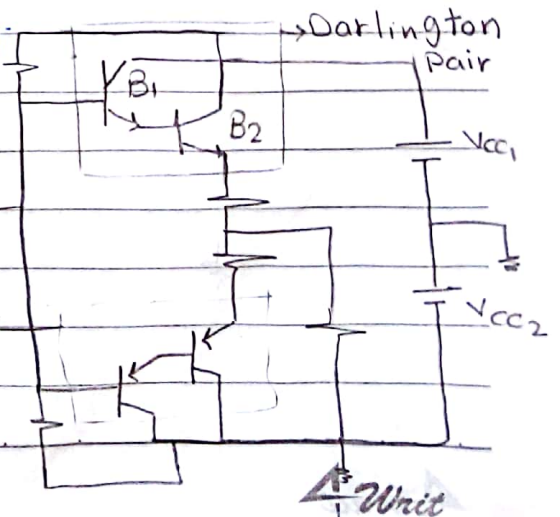

③ Quasi complementary pushpull


ليست التفاضل

The most popular form of power amplifier.

في Basing بين قنار

بين ال V_{in} سغالو بالتي امداد

من هياك ال V_{in} وسينج

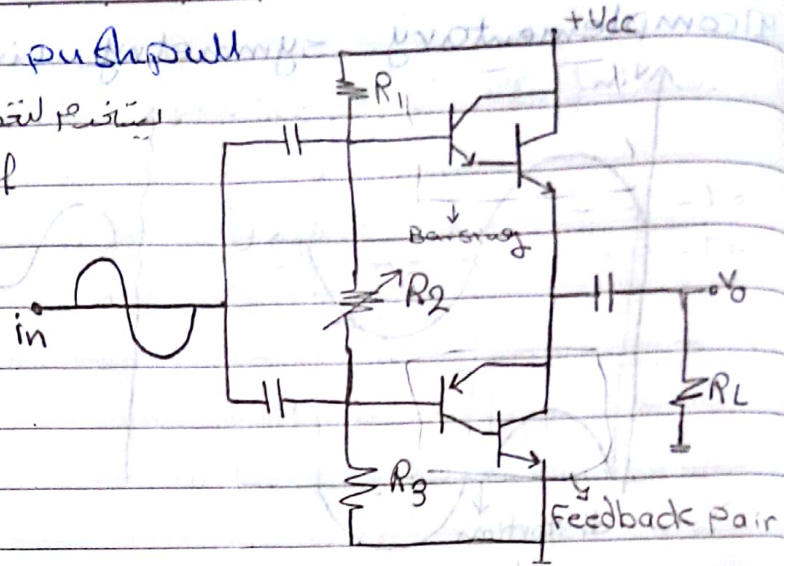

نفس الرسم بس شيل المقاومة المتغيرة وبها

compensating diode.

class AB \rightarrow class B with little Basing

voltage divider / two compensating diode

For class A with transformer coupling.

$$\eta = 50\%$$

$$\eta_{\max} = 50 \left[\frac{V_{CE\max} - V_{CE\min}}{V_{CE\max} + V_{CE\min}} \right]$$

For class B Amplifier

$$\eta_{\max} = 78.54\%$$

$$\eta = 78.54 \times \frac{V_{LP}}{V_{CC}} \%$$

Ex:-


الحرارة تزداد و V_{BE} يزداد وبالتالي يزداد I_C فيتوقظ الجهاز

$$I_C \propto V_{BE}$$

Thermal runaway

$I_C \uparrow \uparrow \uparrow$ يزداد دائما

التيار يزداد في

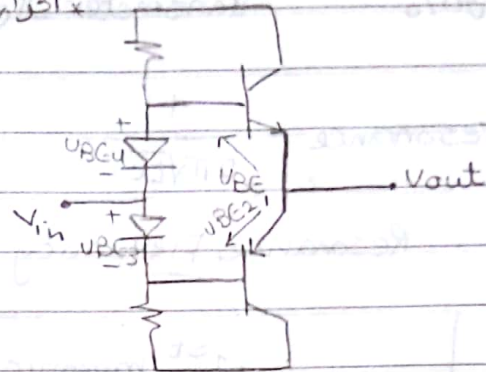

$$V_{BE1} + V_{BE2} - V_{BE3} - V_{BE4}$$

heat dissipation. I_C constant و V_{BE} constant


stable with temperature

what is quiescent collector current?

The max efficiency.

$$I_{Bias} = \frac{V_{CC} - 1.4}{2 \times 3.9} = 2.38 \text{ mA}$$


$$I_C \approx I_B = 2.38 \text{ mA}$$

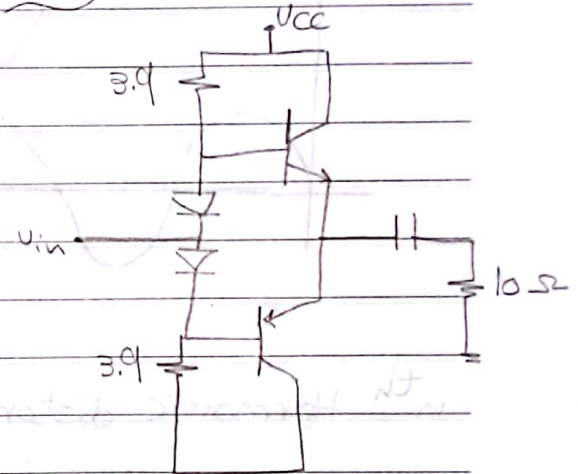

$$I_{C(p)} = \frac{V_{CC}}{2R_C} = \frac{20}{2 \times 10} = 1 \text{ A}$$

$$I_{dV} = \frac{I_{C(p)}}{\pi} = \frac{1}{\pi} = 0.318 \text{ A}$$
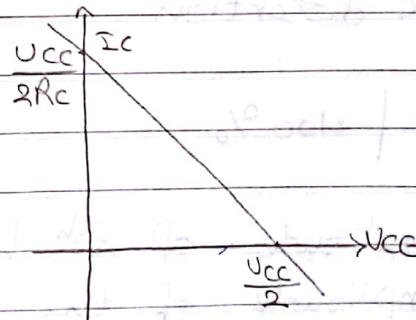
$$\text{total current Drain} = 2.38 + 0.318$$



$$P_{DC} = V_{CC} \times I_{DC} = 20 \times 0.32 = 6.4 \text{ W}$$

$$P_{DC} = \frac{V_{CC}^2}{8R_L} = \frac{(20)^2}{8 \times 10} = 5 \text{ watt}$$

$$\eta = \frac{P_o}{P_i} \times 100 = 78.1\%$$



Class C Amplifier.

$$\eta = 90\%$$

بیشترین راندمان، و موج خروجی آن Transmitter

$$F_{\text{resonance}} = \frac{1}{2\pi\sqrt{LC}}$$

بیشترین فرکانس (RF) Resonance Frequency

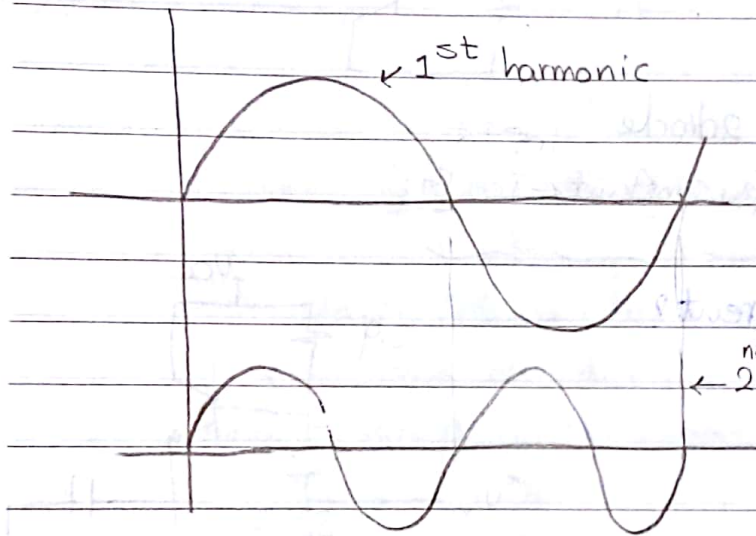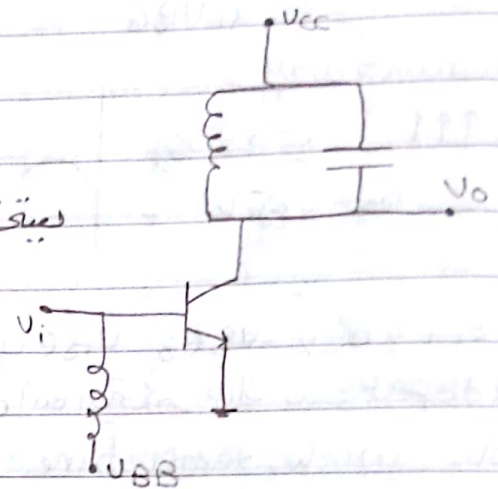

و موج

n^{th} Harmonic distortion

$$D_n = \left| \frac{A_n}{A_1} \right| \times 100\%$$

$A_n \rightarrow$ The Amplitude of n^{th} harmonic

$A_1 \rightarrow$ the Amplitude of the Fundamental

Total harmonic distortion (T.H.D)

$$THD = \sqrt{D_2^2 + D_3^2 + D_n^2} \times 100\%$$


Power Amplifier

Factors affect on power Amplifier:-

$$\eta \uparrow \uparrow = \frac{P_{o(dc)}}{P_{i(dc)}}$$

power dissipation "consumption" \downarrow

impedance matching between Amp o/p, Load

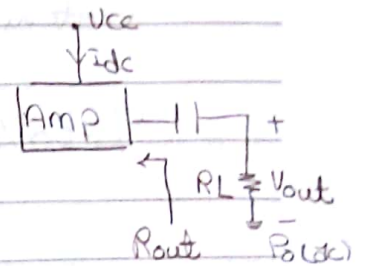

Types of Amp:-

1-A


2-B

3-AB

4-C


5-D

Class A

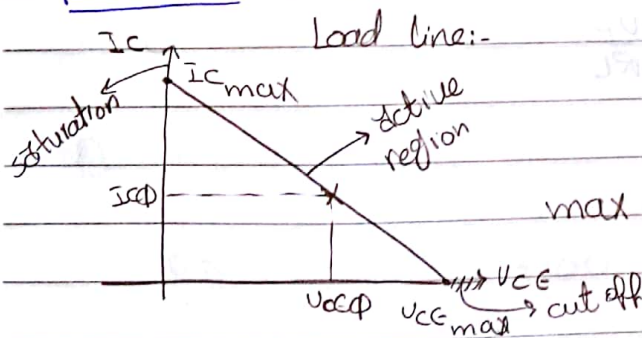

max swing \rightarrow I_c و V_{ce}

max swing و Q point و I_c و V_{ce}

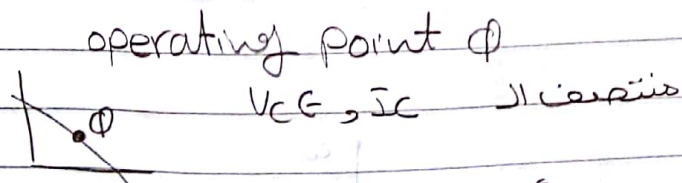

operating cycle $\rightarrow 360^\circ$

$\eta \rightarrow 25\% - 50\%$


$$\eta = \frac{P_{o(dc)}}{P_{i(dc)}}$$

$$P_{i(dc)} = V_{cc} I_{cQ}$$

$$P_{o(dc)} = V_{ce_{rms}} I_{c_{rms}} = \frac{V_p}{\sqrt{2}} \frac{I_p}{\sqrt{2}} = \frac{V_p I_p}{2}$$

$$V_{p_{max}} = V_{cc}/2$$

$$\eta_{max} = 25\%$$

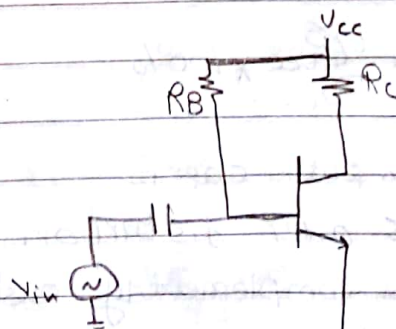

$$R_L = 8R_L$$

(2)


Date

Subject



class A with coupled Transformer.

matching

$$\eta = 50\%$$

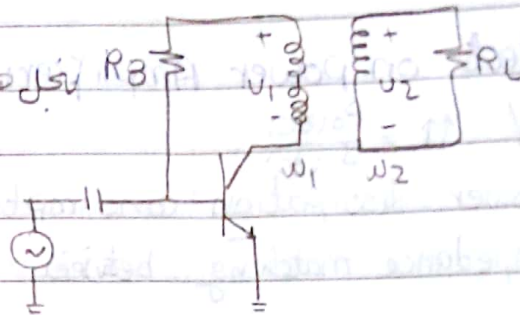

Class B

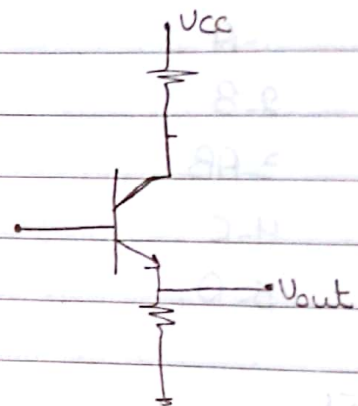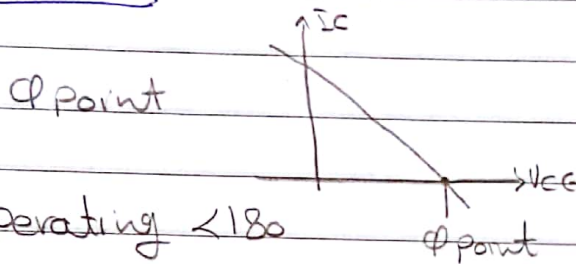

$$\eta = \frac{P_o(d.c)}{P_i(d.c)}$$

$$P_i(d.c) = V_{CC} I_{dc} \quad I_{dc} = \frac{2}{\pi} I_p = \frac{2}{\pi} \frac{V_p}{R_L}$$

$$P_o(d.c) = \frac{V_{rms}^2}{R_L} = \frac{V_L^2 P}{2 R_L}$$


$$\eta = \frac{\pi}{4} \frac{V_L P}{V_{CC}} \times 100\%$$

$$\eta = \frac{\pi}{4} \times \frac{V_{LP}}{V_{CC}} \times 100\%$$

→ push pull class B

cross over distortion

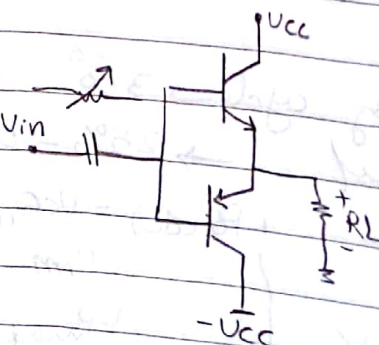using ckt → quasi complementary push pull
→ complementary
→ Transform



12.2 input power

II o/p power

input signal base current $5 \text{ mA} \rightarrow AC$


$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{18 - 0.7}{1.2} =$$

$$\therefore I_{CQ} = \beta I_{BQ}$$

$$P_{in(dc)} = V_{CC} I_{dc}$$

$$I_{C_{rms}} = \beta I_{B_{rms}} = 200 \text{ mA}$$

$$P_{O(dc)} = I_{C_{rms}}^2 R_C$$

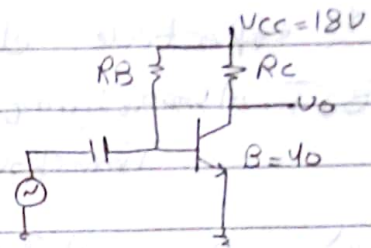


12 ↓ R_B نضبط المقاومة لتتغير I_B

$$I_B \uparrow \rightarrow P_{in} \uparrow$$

$$\eta = \frac{P_O}{P_{in}} \times 100$$

$$25\% = \frac{1.5}{P_{i(dc)}} \times 100$$

$$P_{i(dc)}$$

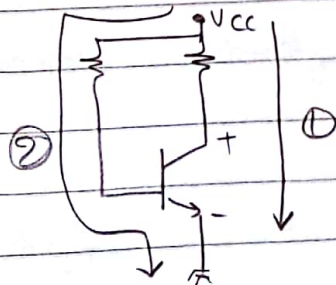

Print لو عاوز اكتبه

$$V_{CC} - I_C R_C = V_{CE} = V_C$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\text{power consumption} = P_{i(dc)} - P_{O(dc)}$$

5] Coupled Transformer


25:1

4 Ω load

SS effective elc load

BJT

Transformer

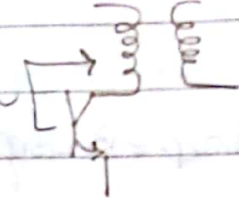

$$\frac{R_L'}{R_L} = \frac{1}{a^2} = \left(\frac{N_1}{N_2} \right)^2$$

$$R_L' = R_L \times a^2$$

6] $R_L = 8$

$$R_L' = 8$$

$$R_L' = \frac{1}{a^2} R_L$$

$$8 \text{ k} = \frac{1}{a^2} 8$$

$$a^2 = 1000$$


$$a = \sqrt{1000}$$

7] $R_L = \frac{16}{4} = 4 \Omega$

$$8 \text{ k} = \frac{1}{a^2} 4$$

$$a^2 = 2000$$

$$a = \sqrt{2000}$$

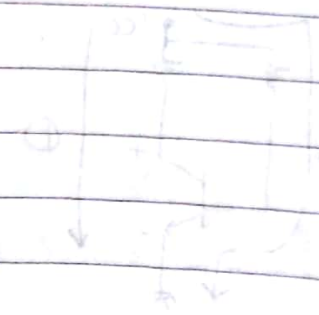

8] Transformer coupled class A

$$R_L = 16 \Omega$$

$$3.87:1$$

$$N_1 : N_2$$

$$V_{CC} = 36 \text{ V}$$

circuit drives 2 W To the load

$$\rightarrow P_{o \text{ dc}}$$


a) P_{dc} across primary

$$P_{dc} = P_{o \text{ dc}} = 2 \text{ W}$$

b) $V_L \text{ dc}$ across Primary

$$P = \frac{V_L^2}{R_L'}$$

$$R_L' = 8^2 R_L$$

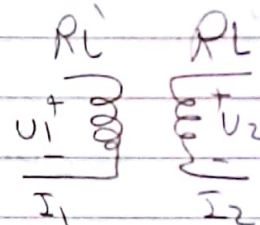

$$V_L^2 = 2 \times (8^2) R_L = 2 \times (3.87) \times 16 =$$

c) $V_L \text{ dc}$

$$P = \frac{V_L^2}{R_L}$$

$$V_L^2 = 2 \times 16 = 32$$

$$V_L = \sqrt{32}$$

d) I_{rms} primary, secondary

$$P_p = I^2 R_L'$$

$$I^2 = 2 / (8^2 R_L)$$

5

19

8-اذا

$$I_{CQ} = 150 \text{ mA}$$

$$\eta =$$

$$\eta = \frac{P_{O(d.c)}}{P_{i(d.c)}} \times 100 = 37\%$$

$$P_{i(d.c)} = V_{CC} \times I_{DC}$$

$$36 \times 150 \text{ mA} =$$

$$P_{O(d.c)} = 2 \text{ watt}$$

110

سٲ

111

سٲ

112 class B

22V peak signal To 8-Ω load

$$V_{CC} = 25V$$

$$P_{in}, P_{O}, \eta$$

$$P_{in} = V_{CC} \times I_{DC}$$

$$25 \times \frac{2}{\pi} \times \frac{V_P}{R_L} = 25 \times \frac{2}{\pi} \times \frac{22}{8}$$

$$P_O = \frac{V_P^2}{2R_L} = \frac{(22)^2}{8}$$

$$\eta = \frac{P_{O(d.c)}}{P_{i(d.c)}} \times 100 = \frac{\frac{\pi}{4} \times \frac{V_P^2}{R_L}}{25 \times \frac{2}{\pi} \times \frac{V_P}{R_L}} = \frac{\pi}{4} \times \frac{22}{25} =$$

(7)

Date: / / Subject:

(13)

$$P_{i(dc)} = V_{CC} \times I_{CQ}$$

$$V_{CC} \times \frac{2}{\pi} \frac{V_P}{R_L}$$

$$\left(\frac{2}{\pi} \right) \times \frac{(25)^2}{8}$$

$$P_{o(dc)} = \frac{V_{CC}^2}{R_L}$$

$$\eta = \frac{\pi}{4} \times \frac{V_{CC}}{V_{CC}} \times 100 = 78.54\%$$

(14)

class B

$$V_{CC} = 22$$

$$R_L = 4$$

$$O/P \text{ voltage peak} = 20$$

$$P_i = V_{CC} \times \frac{2}{\pi} \left(\frac{V_P}{R_L} \right) = 22 \times \frac{2}{\pi} \times \frac{20}{4}$$

$$P_o = \frac{(20)^2}{2 \times 4}$$

116]

class B]

$$\textcircled{a} \max P_{o(dc)} = \frac{V_L^2}{2R_L} = \frac{V_{CC}^2}{2R_L} = \frac{30^2}{2 \times 8} = 56.25 \text{ W}$$

$$\textcircled{b} \max P_{i(dc)} = V_{CC} I_{dc} = V_{CC} \times \frac{2}{\pi} \times \frac{V_{CC}}{R_L} = \frac{2V_{CC}^2}{\pi R_L}$$

$$= \frac{2 \times 30^2}{\pi \times 8} = 71.6197 \text{ W}$$

$$\textcircled{c} \eta = \frac{P_{o(dc)}}{P_{i(dc)}} = \frac{56.25}{71.619} \times 100\% = 78.5398\%$$

$$\Rightarrow \textcircled{d} P_o = \frac{2V_{CC}^2}{\pi^2 R_L} = \frac{2(30)^2}{\pi^2 \times 8} = 22.797 \text{ W}$$

117]

$$P_i = V_{CC} \times I_{dc} = V_{CC} \times \frac{2}{\pi} \frac{V_p \rightarrow V_{rms} \sqrt{2}}{R_L}$$

$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

$$P_i = 30 \times \frac{2}{\pi} \times \frac{8\sqrt{2}}{8} = 27.0094 \text{ W}$$

$$P_o = \frac{V_{rms}^2}{R_L} = \frac{8^2}{8} = 8 \text{ W}$$

$$\eta = \frac{P_o}{P_i} = \frac{8}{27.009} \times 100\% = 29.6192\%$$

$$\Rightarrow P_{2\phi} = P_i - P_o$$

$$= 27.0094 - 8 = 19.0094 \text{ W}$$

* op. amp

I] A_{vd} differential oplooping:


$$V_o = (V^+ - V^-) A_{vd}$$

$$\text{ideally } A_{vd} = \infty$$

$$\left(\begin{array}{l} g_{din} \times BW = \text{const} \\ R_F \rightarrow \infty \end{array} \right)$$

(adv of R_F)

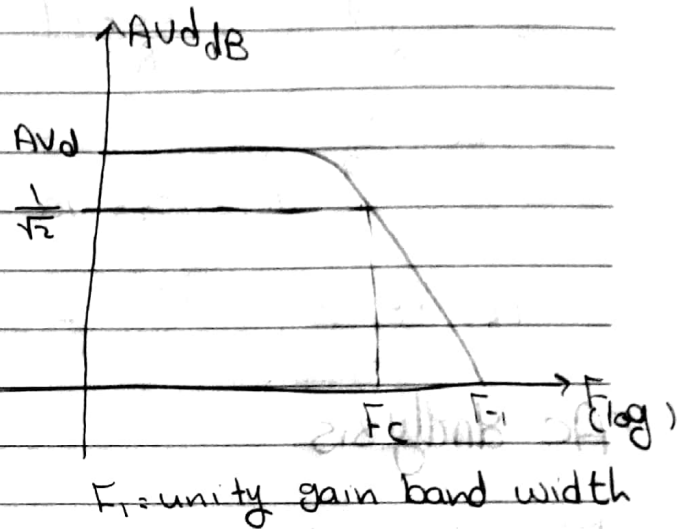1. Reduce g_{din} (under control)
2. increase Band width
3. increase R_{in}
4. Decrease R_o



II] A common mode:

noise is, because 2 input diff



ideal $\rightarrow 0$

in practice \rightarrow very small

$$CMRR = 20 \log \frac{A_{vd}}{A_{cm}}$$

$$CMRR = \frac{\infty}{0} = \infty \leftarrow \text{ideal}$$

Differential amplifier

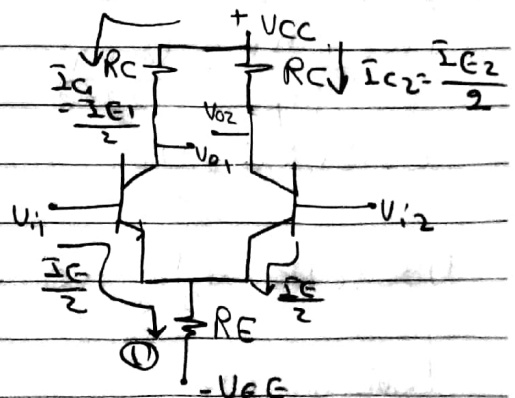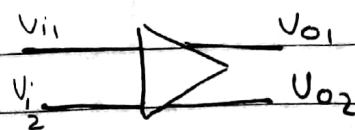

Dc analysis:-

kul 1.

$$V_E = 0 \quad V_{BE} = -0.7 \text{ V}$$

$$I_E = \frac{V_E - (-V_{EE})}{R_E} = \frac{V_{EE} - 0.7}{R_E}$$

$$I_{C1} = I_{C2} = \frac{I_E}{2}$$

$$V_{C1} = V_{C2} = V_{CC} - I_C R_C = V_{CC} - \frac{I_E}{2} R_C$$

$$r_e = \frac{26 \text{ mV}}{I_E}$$

Ac analysis

Single ended $V_{i2} = 0$

Assume that ϕ_1, ϕ_2 are well matched.

$$I_{b1} = I_{b2} = I_b$$

$$r_{i1} = r_{i2} = r_i = \beta r_e \rightarrow \text{From dc analysis}$$

For simplification

$$R_E = \infty$$

Partial circuit for calculating i_b

applying kul.

$$V_{in} - r_i I_b - r_i I_b = 0$$

$$I_b = \frac{V_{in}}{2 r_i} = \frac{V_{in}}{2 \beta r_e}$$

$$\beta_1 = \beta_2 = \beta$$

$$I_C = \beta I_b = \frac{V_{in}}{2 r_e}$$

$$V_o = I_C R_C = \frac{V_{in}}{2 r_e} R_C = \frac{R_C}{2 r_e} V_{in}$$

of ϕ_1, ϕ_2

single ended voltage gain

$$A_V = \frac{V_O}{V_i} = \frac{R_C}{2r_e}$$

AV of one stage in cm-Amp

Net the AV of cm-Amp total:

III

$$V_O = I_C R_C = \frac{V_i}{2r_e} R_C$$

$$\beta = 75$$


$$r_{i1} = 20k\Omega$$

$$r_i = \beta r_e$$

$$20 \times 10^3 = 75 r_e$$

$$r_e = 266.6 \Omega$$
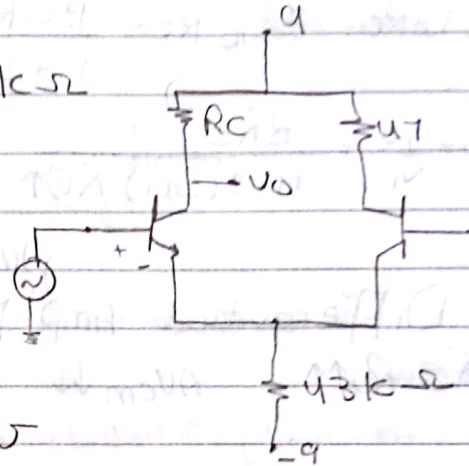
$$V_O = \frac{2 \times 10^{-3}}{2 \times 266.6} \times 47 \times 10^3 = 0.17V$$



II/ Double ended AC voltage gain

By similarity



$$A_d = \frac{V_O}{V_d} = \frac{R_C}{r_e}$$

ناتج الجهد

$$V_d = V_{i1} - V_{i2}$$

III/ Common mode

AC model.

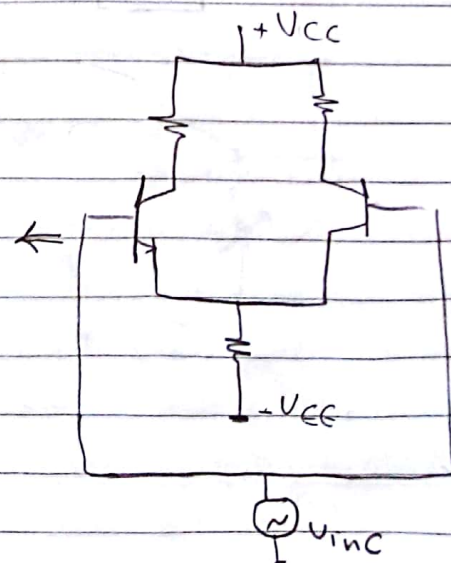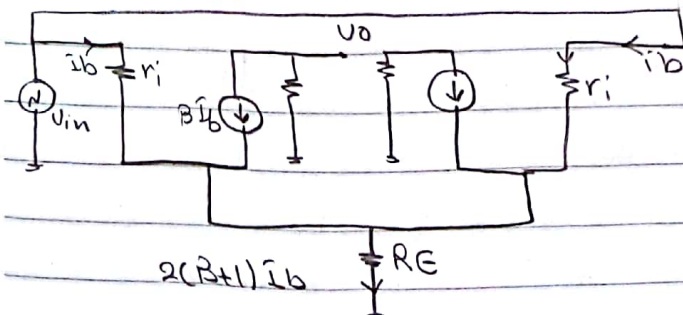

Write

$$I_b = \frac{U_i}{r_i + 2(B+1)R_E}$$


$$I_b = \frac{U_i}{r_i + 2(B+1)R_E}$$

$$U_o = I_c R_c = \beta I_b R_c = \frac{\beta U_i R_c}{r_i + 2(B+1)R_E}$$

$$\downarrow A_v = \frac{U_o}{U_i} = \frac{\beta R_c}{r_i + 2(B+1)R_E} \uparrow$$

مقدار A_v بزرگتر

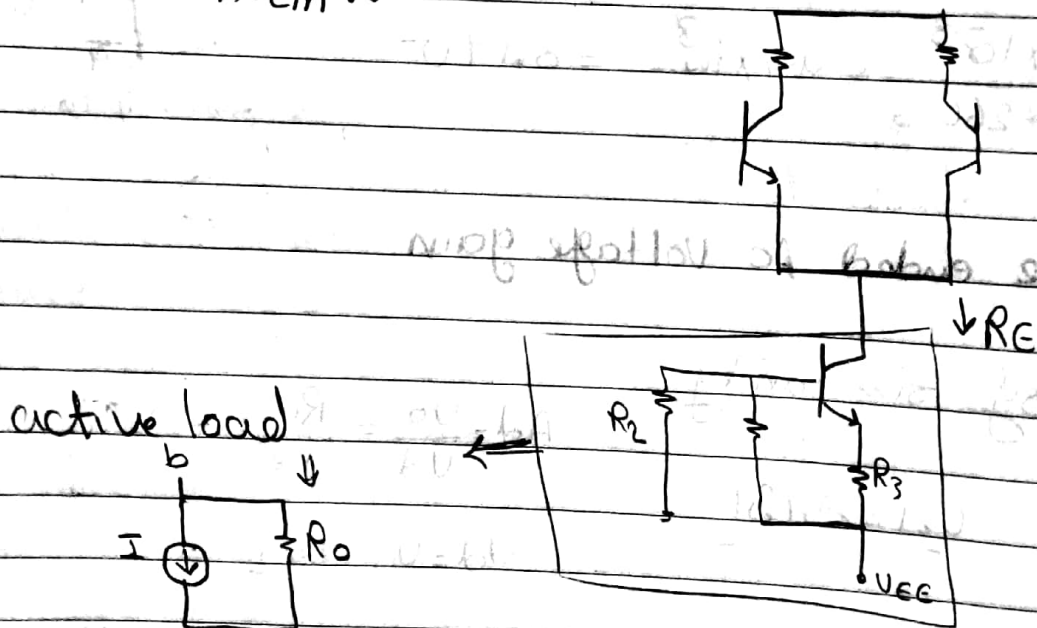تاثیر R_E بزرگتر \rightarrow A_v کوچکتر
 Differential Amplifier with constant current source
 $R_E = R_o \uparrow$ $A_{vcm} \downarrow$



op-amp specifications - Dc offset parameters


offset current and Voltage:-

Offset voltage

idealy $V_{offset} = 0$

Practice $\approx 26 \text{ mV}$

تأثير ال stage اخلية

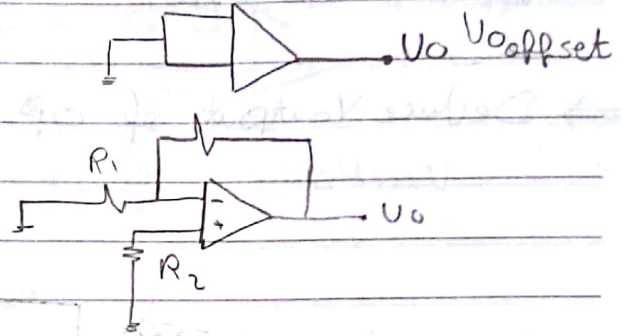

$V_{offset} \rightarrow$




Data Sheet.

V_{offset}

التيار ال اخلية ال اخلية ال اخلية ال اخلية ال اخلية

$$V_o = (1 + \frac{R_F}{R_1}) V_{in}$$


\leftarrow

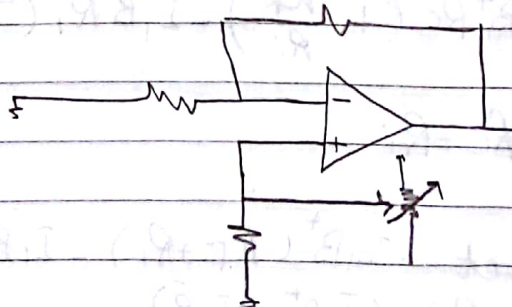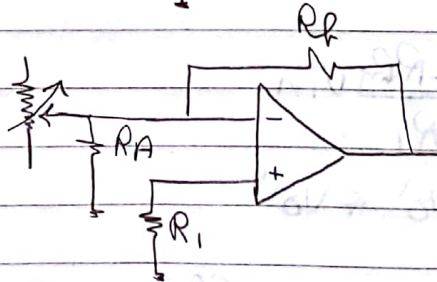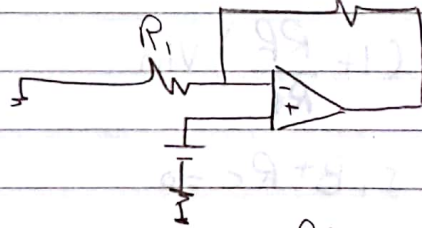


② offset current

$$I_{Bias} = \frac{I_{B^+} + I_{B^-}}{2}$$

$$I_{offset} = I_{B^+} - I_{B^-}$$

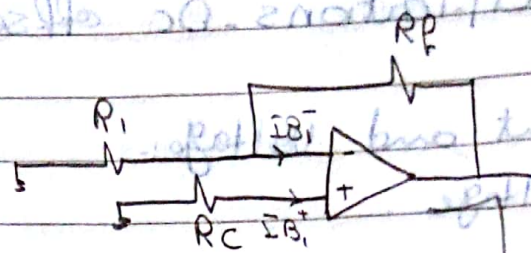

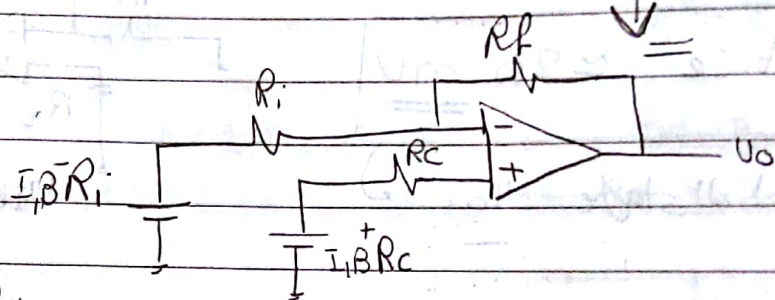⇒ Deduce V_{out} of op-amp due to I_{offset}



$$V_o' \Rightarrow I_{B^-}R_i = 0$$

$$V_o' = \left(1 + \frac{R_F}{R_i}\right) V_{in}$$

$$V_o'' \Rightarrow I_{B^+}R_C = 0$$

$$V_o'' = -\frac{R_F}{R_i} V_{in}$$

$$V_o = V_o' + V_o''$$

$$V_o = I_{B^+}R_C \left(1 + \frac{R_F}{R_i}\right) - I_{B^-}R_i \left(-\frac{R_F}{R_i}\right)$$

$$R_C = R_i$$

$$\begin{aligned} V_{offset} &= I_{B^+}(R_F + R_i) - I_{B^-}R_F \\ &= R_F (\underbrace{I_{B^+} - I_{B^-}}_{I_{offset}}) \end{aligned}$$


$$V_{offset} = I_{offset} R_F$$

$$V_{offset} = V_{offset \text{ due to } V_{I0}} + V_{offset \text{ due to } I_{I0}}$$

Find the total offset voltage for the circuit if

$$V_{I0} = 4 \text{ mV}$$

$$I_{I0} = 150 \text{ nA}$$

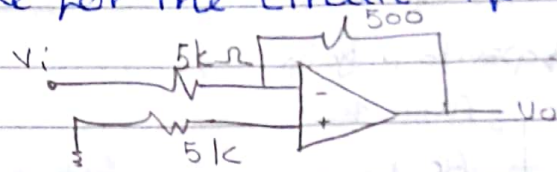

$$V_{offset \text{ due to } V_{I0}} = V_{I0} \left(1 + \frac{R_F}{R_i} \right) = 4.04 \text{ mV}$$

$$V_{offset \text{ due to } I_{I0}} = I_{I0} R_F$$

$$V_{offset} = \boxed{} + \boxed{}$$

$$I_{IB}^+ = I_{IB} + \frac{I_{I0}}{2}$$



$$I_{IB}^- = I_{IB} - \frac{I_{I0}}{2}$$

Op-amp


Differential amplifier

$$V_o = A_d (V^+ - V^-)$$


$A_d \rightarrow$ open loop gain

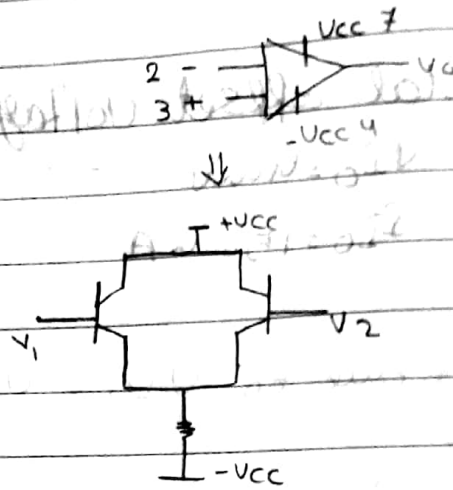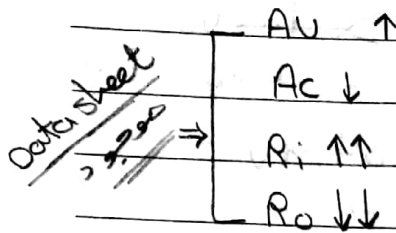

Op-amp with Feedback

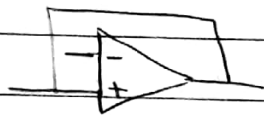



+ve Feedback
oscillator

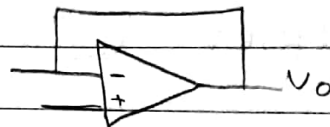

-ve Feedback
amplifier

$A_{cl} \rightarrow$ closed loop gain.

with Feedback

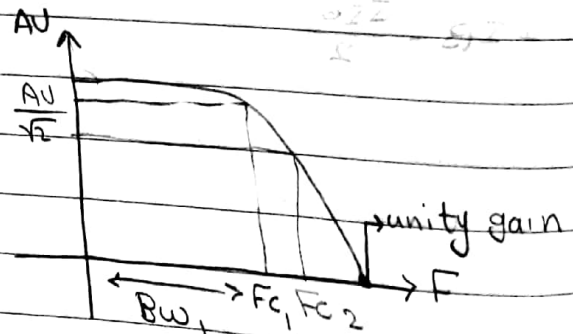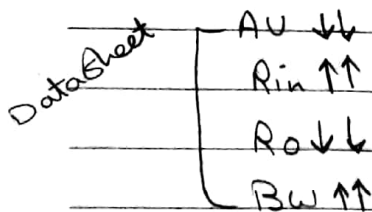

Gain Bandwidth product:



$$A_v * BW = \text{constant}$$

$$A_v \propto \frac{1}{BW}$$


$$F_{c1} \rightarrow BW_1$$

$$F_{c2} \rightarrow BW_2 \uparrow \uparrow$$


input signal models:-

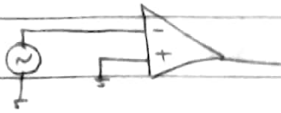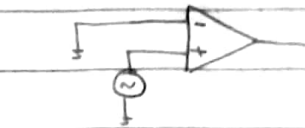ch 11 255 Q18

single ended

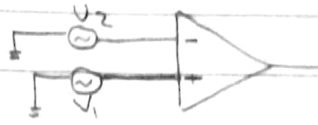

Double ended

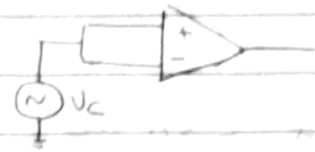

$$V_o = A_c V_c$$

common mode.

A_{CM} ↓

Ex: noise

op-amp specifications:-

I_{offset} → offset voltage
 → offset current

Common mode rejection ratio:-

~~Ad~~


$$A_c \rightarrow V_o = A_c V_c$$

$$A_d \rightarrow V_o = A_d V_d$$

$$CMRR = \frac{A_d}{A_c} \rightarrow 20 \log \frac{A_d}{A_c}$$

dB

$$\text{slow rate} = \frac{\Delta V_{out}}{\Delta t}$$

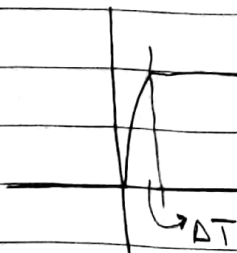 Δt

slow rate

Slope (linear)

Slope (slow)

Write

5,6,7

Non inverting

Sheet

24,17


Date

Subject

11

$$U_o = -\frac{R_F}{R_i} V_{in}$$

12

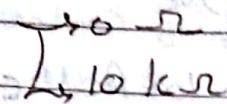

$$U_{o1} = -\frac{R_F}{R_i} V_{in}$$

$$A_V = -\frac{R_F}{R_i} = -\frac{500}{10} = -50$$

$$U_{o2} = -\frac{R_F}{R_i'} V_{in}$$

$$A_V = -\frac{R_F}{R_i'} = -\frac{500}{20} = -25$$

$$-\frac{500}{20} < A_V < -\frac{500}{10}$$

$$-25 < A_V < -50$$

13

$$U_o = -\frac{R_F}{R_i} V_i$$

$$2 = \frac{-1 \times 10^5}{20 \times 10^3} V_i$$

$$V_i = -2$$

$$U_o = -\frac{R_F}{R_i} V_{in}$$

$$= -\frac{200}{20} V_i$$



$$U_o = -1$$

$$U_o = -5$$

8]

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

9]

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

11]

$$V_o = V_i$$


matching, buffer

$$V_o = \left(1 + \frac{R_f}{R_1} \right) V_{in}$$

$$R_f = 0 \text{ s.c}$$

$$R_1 = \infty \text{ o.c}$$

$$V_o = (1 + 0) V_{in}$$

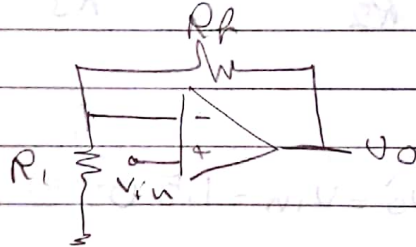

6] sketch

integrator

$$\frac{-1}{R_c} \int V_i(t) dt$$

$$V_o = \frac{-1}{200k \times 0.1 \mu} \int 1.5 dt$$

$$\frac{-1.5}{R_c} t$$

$$\frac{-1.5}{R_c}$$

V_{in}

1.5V

V_o

t


t

Writ

✓ 1500

$$V_0 = V_1 - 2V_2 + 3V_3$$

Design by 2 op-amp

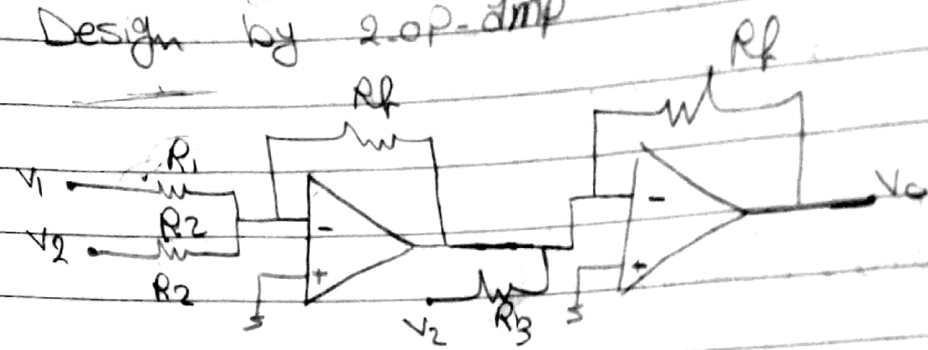

$$\frac{R_F}{R_1} = 1$$

$$\frac{R_F}{R_2} = 2$$

$$\frac{R_F}{R_3} = 3$$

[12]

$$V_0 = V_{in} = 1.5 \text{ V}$$

$$V_0 = \frac{-R_F}{R_1} V_0 = \frac{-100}{20} \times 1.5$$

$$[13] \quad V_{01} = \left(1 + \frac{400}{20}\right) \times 0.1$$

$$V_{02} = V_i = 1 \text{ V}$$

$$V_0 = -\left[\frac{R_F}{20} V_{01} + \frac{R_F}{10} V_{02}\right]$$

$$[14] \quad V_0 = 0.2 \text{ V}$$

$$V_2 = \frac{-200}{20} \times 0.2$$

$$V_3 = \left[1 + \frac{200}{10}\right] \times 0.2$$

Write

115

$$V_{o1} = - \left[\frac{600}{15} \times 0.25 \text{ mV} - \frac{600}{30} \times 0.20 \text{ mV} \right]$$

$$V_{o2} = -20 \text{ mV}$$

$$V_o = - \left[\frac{300}{30} \times V_{o1} + \frac{300}{15} \times V_{o2} \right]$$

116

$$\text{CMRR} = 20 \log \frac{A_d}{A_c}$$

$$A_d = \frac{V_o}{V_{id}} = \frac{20 \text{ mV}}{1 \text{ mV}}$$

$$A_c = \frac{V_o}{V_c} = \frac{20 \text{ mV}}{1 \text{ mV}}$$

116

$$V_{o_{\text{off}}} = V_{o_{\text{offset}}} + V_{o_{\text{offset}}}$$

$$\begin{array}{cc} \downarrow V_{io} & \downarrow I_{io} \\ A V_{io} & I_{io} R_P \\ \downarrow & \\ (1 + \frac{R_P}{R_i}) & \end{array}$$

24


Op-Amp Frequency Parameters

$$\text{Gain} \times \text{BW} = \text{const}$$

$$F_T = B = \text{unity gain BW}$$


$$F_T \times 1 = A_{VO} \times F_c$$

$$F_T = A_{VO} \times F_c$$

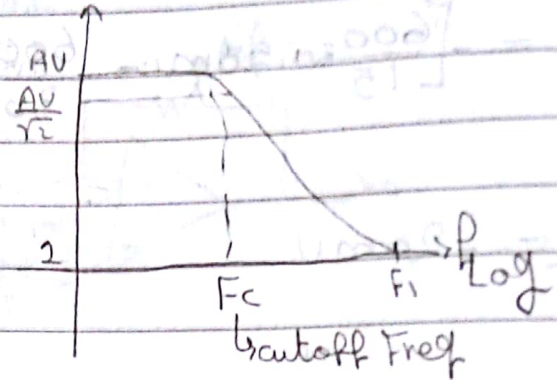

slow rate

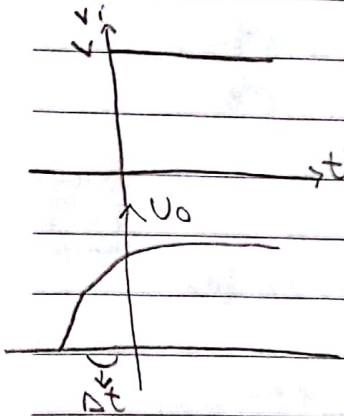:- max rate at which op-amp output can change (V/μs)



$$SR = \frac{dV_o}{dt} \text{ (V/μs)}$$

problem:- an-amp $SR = 2 \text{ V/μs}$ what is the max closed loop voltage gain that can be used when the input signal varies by 0.5 V in 10 μs

$$A_{Vc} \times V_{in} = V_{out}$$

$$A_{Vc} \frac{dV_i}{dt} = \frac{dV_o}{dt}$$

$$A_{Vc} = \frac{dV_o}{dt} \cdot \frac{dt}{dV_i} = 2 \times \frac{10}{0.5}$$

maximum signal frequency:-

$$V_o = k \sin(2\pi F t)$$


$$\frac{dV_o}{dt} = 2\pi F k \cos(2\pi F t)$$

$$\left. \frac{dV_o}{dt} \right|_{\max} = 2\pi F k \leq \frac{1}{R} \quad (\text{for no distortion})$$

$$F \leq \frac{1}{2\pi k R}$$

$$F_{\max} = \frac{1}{2\pi k R} \quad \leftarrow \underline{\underline{f_{max}}}$$

problem:-

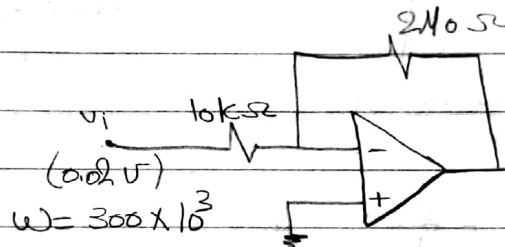

$$V_o = V_{in} \times \frac{-R_f}{R_i} = 0.02 \times \frac{240}{10} = 0.48 \text{ V}$$


$$F_{\max} \leq \frac{1}{2\pi k R}$$

$$\omega \leq \frac{1}{k R} = 1.1 \times 10^6 \text{ rad/s}$$

Differential and common mode operation

Differential inputs

$$V_d = V_{in1} - V_{in2}$$

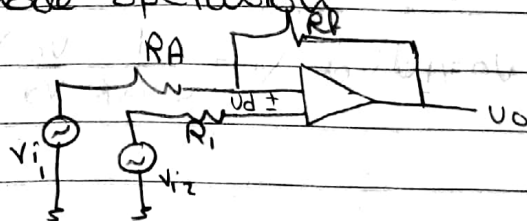

$$V_{od} = A_d V_d$$

common inputs

$$V_c = \frac{1}{2} [V_{i1} + V_{i2}]$$

$$\text{output} = A_d V_d + A_c V_c$$

Q. How measure A_V , A_V in lab

$$V_d = 0.5 - (-0.5) = 1 \text{ mV}$$

$$V_c = \frac{1}{2}(0) = 0$$

$$V_o = A_d V_d + 0$$

$$A_d = \frac{8}{1 \text{ mV}} = 8000$$

$$\text{dB} = 20 \log \frac{8}{1000}$$

$$V_d = 0$$

$$V_c = 1$$

$$A_c = \frac{V_o}{V_c} = \frac{12 \text{ mV}}{1 \text{ mV}} = 12$$

$$\text{CMRR} = \frac{A_d}{A_c} = \frac{8000}{12} = 666.7$$

$$\text{CMRR} \text{ dB} = 20 \log \frac{8000}{12} = 56.48 \text{ dB}$$

deduce the relation between V_o , CMRR

$$V_d A_d + V_c A_c = V_o$$

$$V_o = A_d V_d \left(1 + \frac{V_c A_c}{V_d A_d} \right)$$

$$V_o = A_d V_d \left(1 + \frac{1}{\text{CMRR}} \frac{V_c}{V_d} \right)$$

determine output voltage of op-amp, for $V_{i1} = 150 \mu V$

$$V_{i2} = 140 \mu V$$

$$A_d = 4000$$

$$CMRR = 100$$


$$V_d = V_{i1} - V_{i2} = 150 - 140 = 10 \mu V$$

$$V_c = \frac{1}{2} [V_{i1} + V_{i2}] = 145 \mu V$$

$$V_o = A_d V_d \left[1 + \frac{1}{CMRR} \cdot \frac{V_c}{V_d} \right]$$

Application

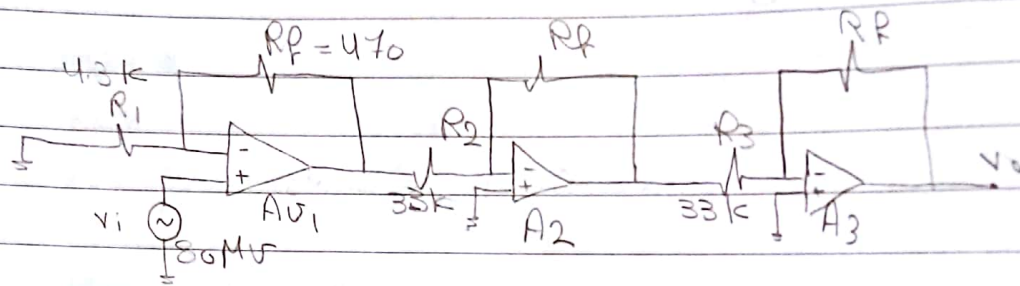- 1) Inverting and noninverting Amplifier
- 2) summation
- 3) sub
- 4) integration
- 5) differentiation
- 6) multiple stage




$$A_V = \frac{V_o}{V_i} = A_1 A_2 A_3 \quad \text{ratio}$$

$$A_V = A_1 + A_2 + A_3 \quad \text{dB}$$

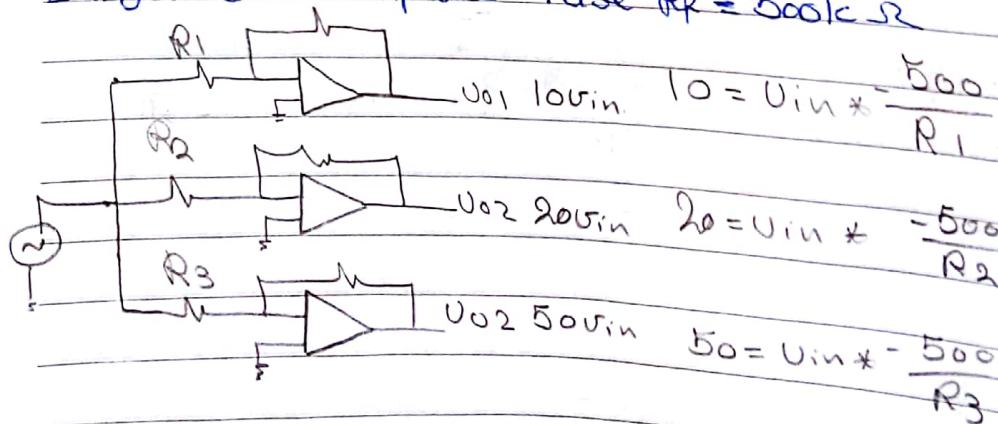problem 1.

Show the connection of three op-amps stage LM348 IC to provide outs that are 10, 20, 50 times larger than inputs. use $R_F = 500k\Omega$




using op amp as a controlling circuit

→ voltage
→ current


controlled sources

I Voltage controlled voltage source.

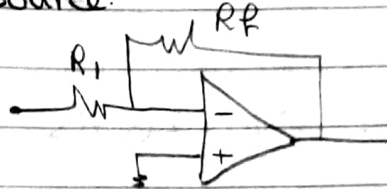


$$V_o = -\left(\frac{R_F}{R_i}\right) V_i$$

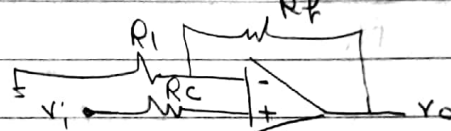
$$V_o = \left(1 + \frac{R_F}{R_i}\right) V_i$$



II voltage controlled current source.

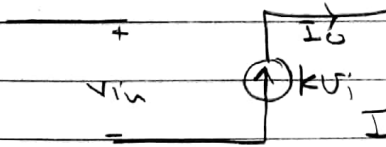


$$I_o = k V_i$$

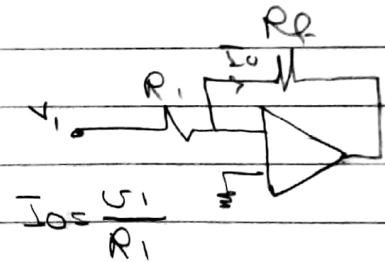


$$I_o = \frac{V_i}{R_i}$$

III current controlled voltage source.

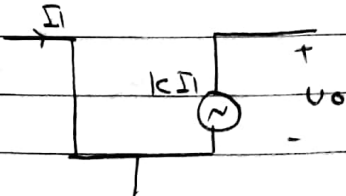


$$V_o = k I_i$$

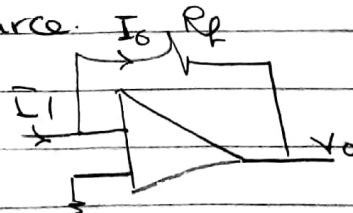


$$-V_o = I_o R_F \quad V_o = -I_o R_F$$

IV current controlled current source.

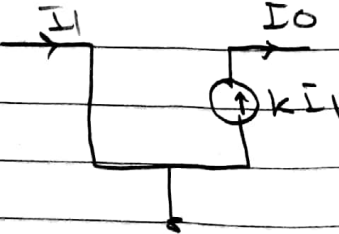

$$I_o = k I_i$$

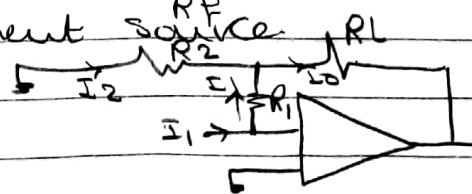


$$I_o = I_1 + I_2$$

$$I_o = I_1 + I_1 \left(\frac{R_1}{R_2}\right)$$

$$I_o = I_1 \left(1 + \frac{R_1}{R_2}\right) = k I_1$$

DC millimeter:

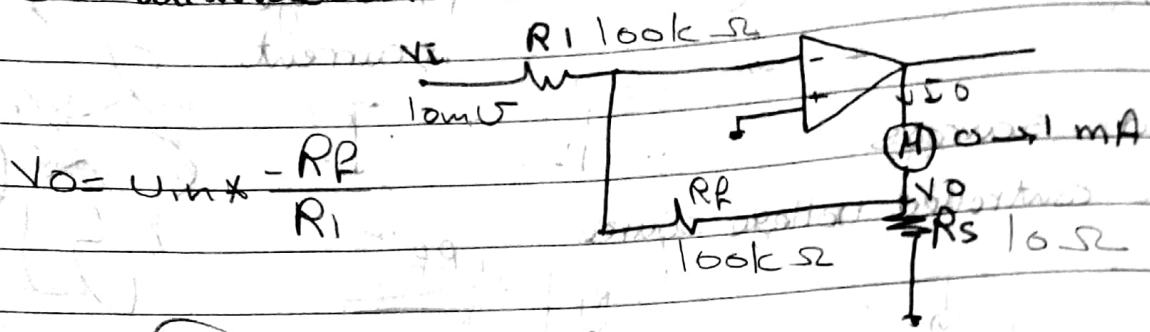

$$V_0 = V_{in} \times \frac{R_f}{R_i}$$

$$I_0 = \frac{V_0}{R_S}$$


$$V_0 = I_0 R_S$$

$$I_0 = \frac{V_{in}}{R_S} \times \frac{R_f}{R_i}$$

① Dc millimeter


Scale small
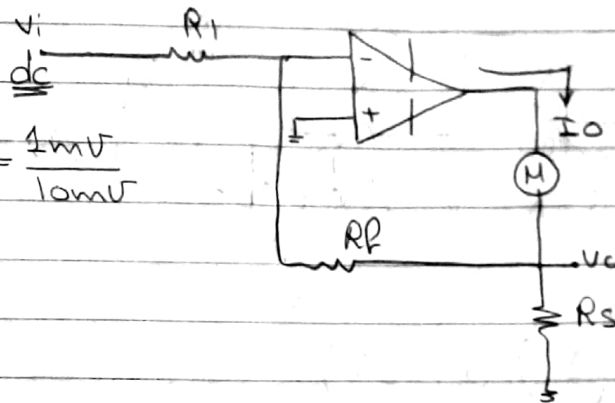
$$\frac{I_o}{V_o} = \frac{R_F}{R_1} \left(\frac{1}{R_S} \right) = \frac{1 \text{ mV}}{10 \text{ mV}}$$




② AC millimeter

Smoothing ← أزالة التموج
→ ripple

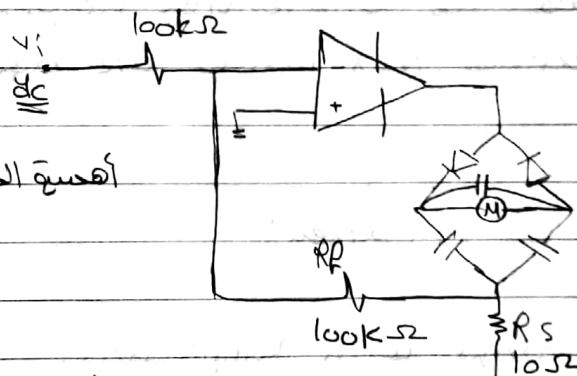


نستخدمه الدوائر في اجهزة الديو دو و ج ١5 Transistor, switch

③ Display Driver

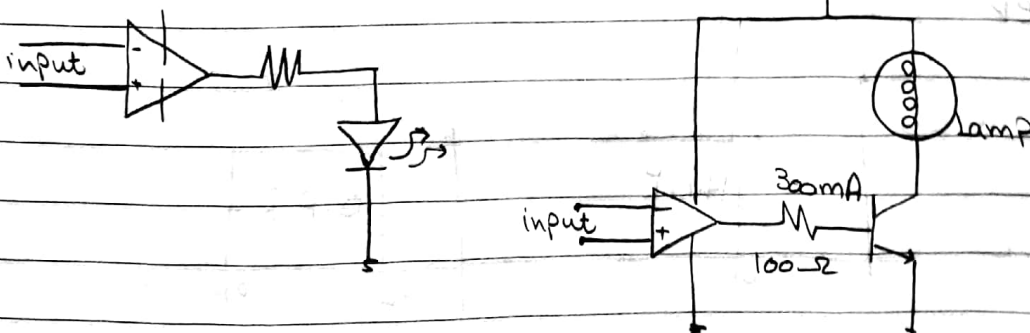

④ instrumentation amplifier

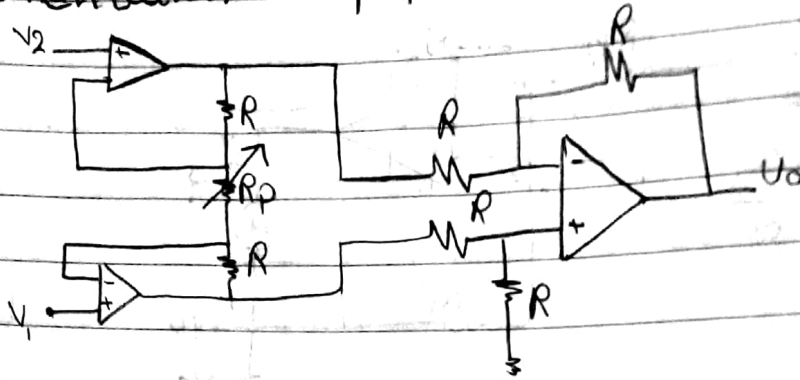


$$V_o = \left(1 + \frac{2R}{R_p}\right)(V_1 - V_2)$$

Deduce \rightarrow properties

\rightarrow it resembles the Differential amplifier with the main difference that inputs are buffered by two op amps


- \rightarrow Low input bias current
- \rightarrow High CMRR
- \rightarrow low offset drift with temperature.

Active Filter

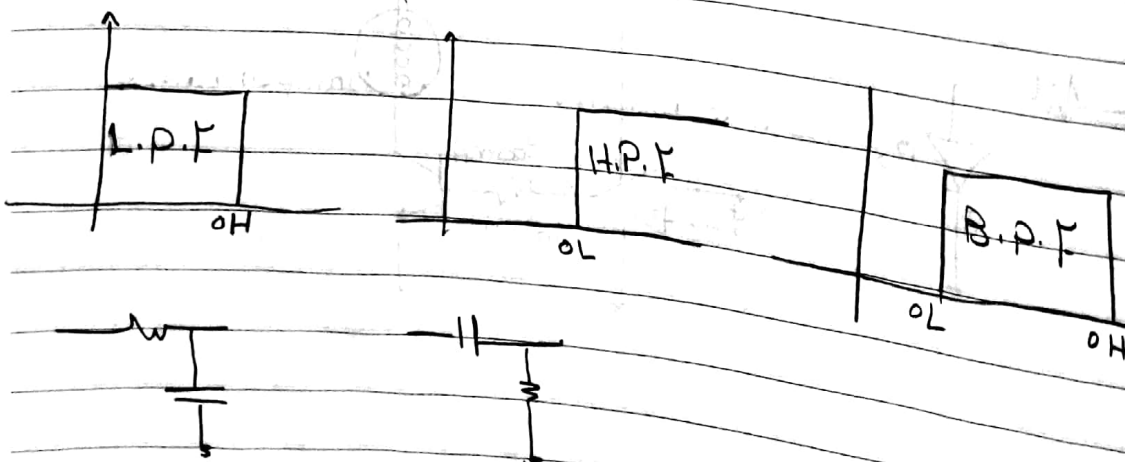


First order L.P.F

$$F_{OH} = \frac{1}{2\pi R_1 C}$$

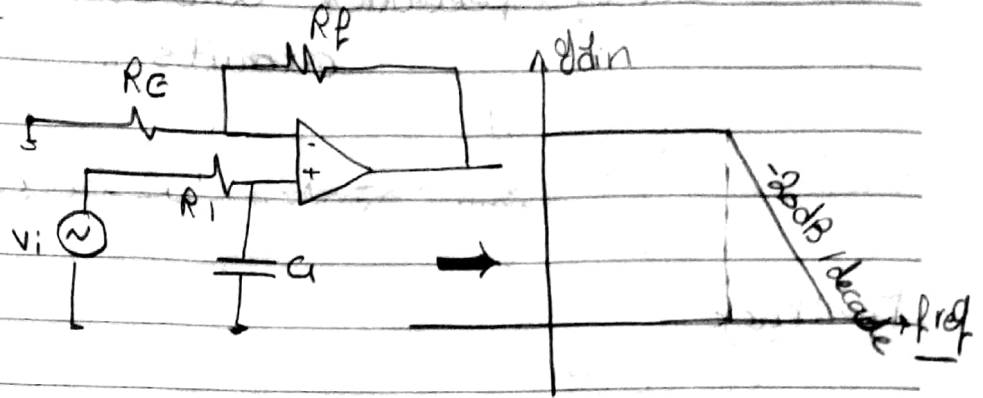


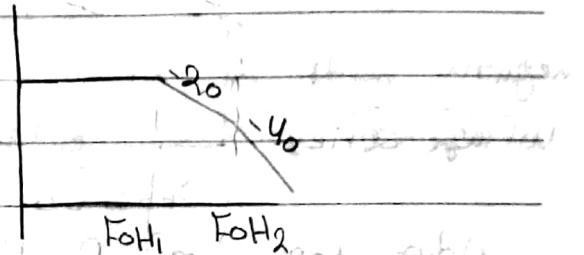Second order \rightarrow (2. first order)



H.P.F ✓

B.P.F

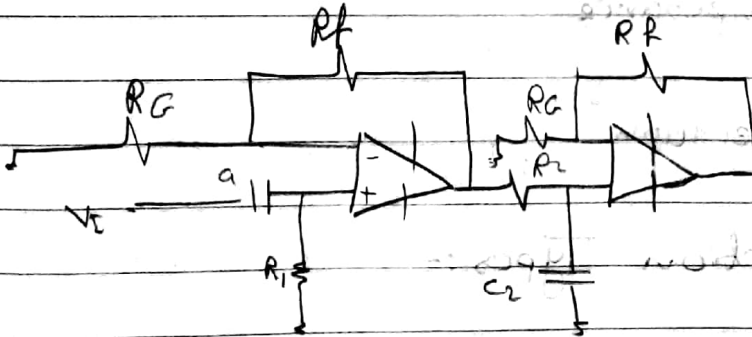


توضیحات ال H.P مع L.P و فیلترهای دیگر

ch 14 Feedback and oscillator circuits

input \rightarrow mixer \leftarrow oscillator

Feedback

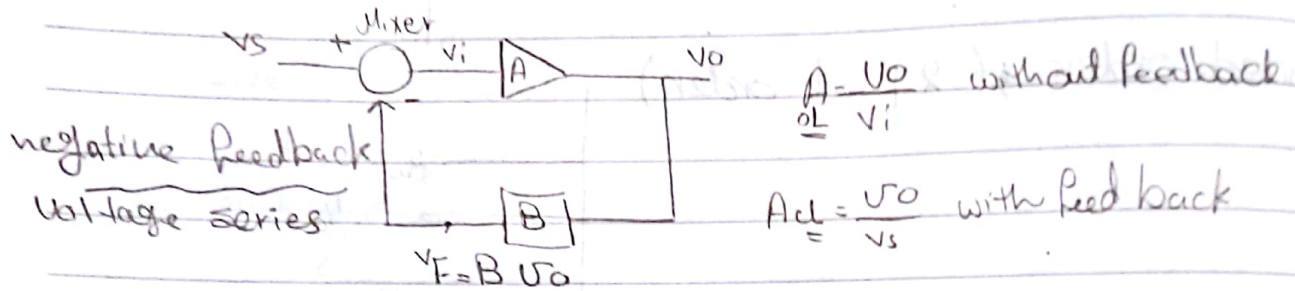

Advantages of Feedback

- \rightarrow Higher input impedance
- \rightarrow Better stabilized voltage gain
- \rightarrow Improved frequency response
- \rightarrow Lower output impedance
- \rightarrow Reduce noise
- \rightarrow more linear operation

Feedback connection Types:-

1. voltage series feedback
2. voltage shunt feedback
3. current \sim
4. current series \sim

1. refers to connecting the output voltage as input to the feedback network.

2. current refers to tapping off some output current through the feedback network.

21-22-23

الاسات
بالتاريخ
الاسات





Date



Subject

→ **series** refers to connecting the feedback signal in series with the input signal voltage.

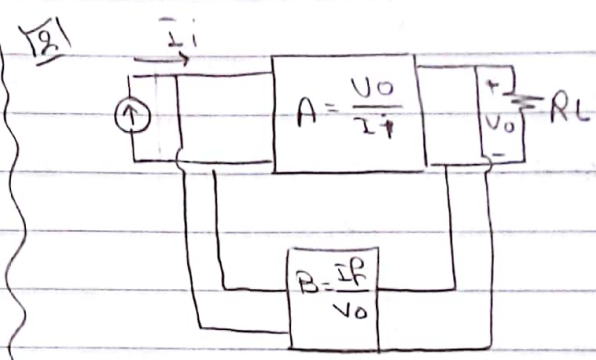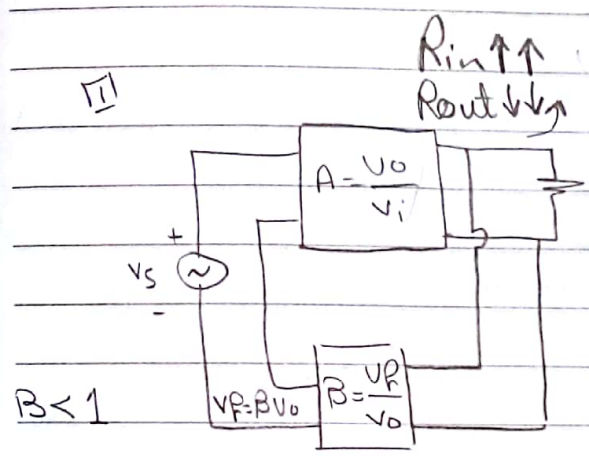→ **shunt** refers to connecting the feedback signal in shunt with an input current source.



دو احسن نوع

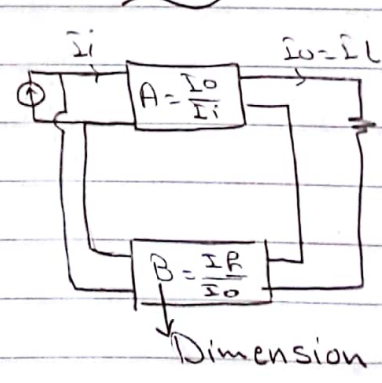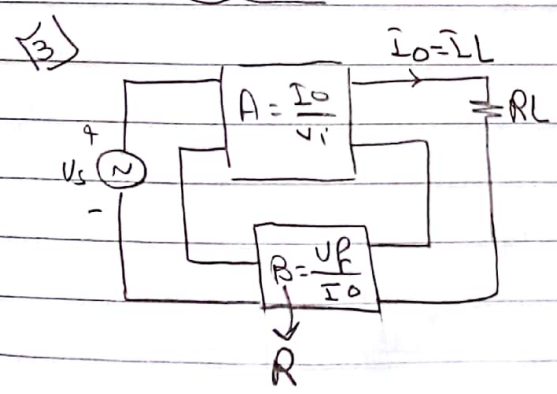

voltage-series

voltage-shunt

current-series

current-shunt

gain A without	$\frac{V_o}{V_i}$	$\frac{V_o}{V_i}$	$\frac{I_o}{V_i}$	$\frac{I_o}{I_i}$
B	$\frac{V_f}{V_o} B V_o$	$\frac{I_f}{V_o}$	$\frac{V_f}{I_o}$	$\frac{I_f}{I_o}$
gain A with	$\frac{V_o}{V_s}$	$\frac{V_o}{I_s}$	$\frac{I_o}{V_s}$	$\frac{I_o}{I_s}$


Write

18) $f_c = ??$

$B_1 = 800k \Omega$

$A_{vcl} = 150 V/mV$

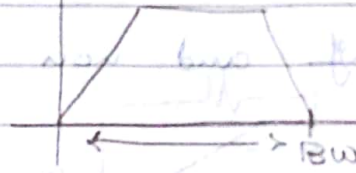$G_{din} \times B_{W} = \text{const} (\beta)$
 $\downarrow = f_c$



19) $SR = 2.4 V/\mu s$

$A_{cl} = \frac{SR}{dv/dt} = \frac{2.4 \times 10^{-6}}{0.3/10 \times 10^{-6}}$

21)

$V_{offset} = V_{offset} + V_{offset}$
 $\downarrow \quad \downarrow$
 $I_o \quad I_o$


$= \left[1 + \frac{R_F}{R_i} \right] V_{I_o} + I_{I_o} R_F$

22)

$A_{cl} = \frac{-R_F}{R_i}$

$Z_i = R_i$


$Z_o = R_o / (1 + A\beta)$

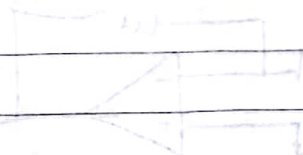


Handwritten notes and scribbles at the bottom of the page.

CH4: op-amp application:-

I Inverting and non inverting.

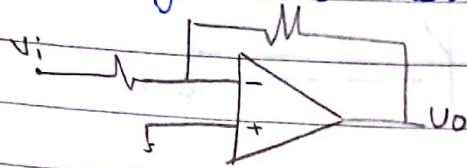

$$A_v = -\frac{R_f}{R_i}$$

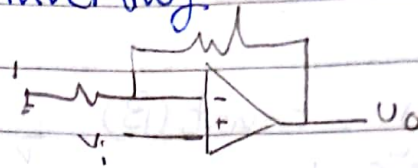

$$A_v = \left(1 + \frac{R_f}{R_i}\right)$$


② Buffer

$$R_f = \text{S.C } \infty$$

$$R_i = \text{O.C } \infty$$

$$A_v = 1$$

③ summing , difference

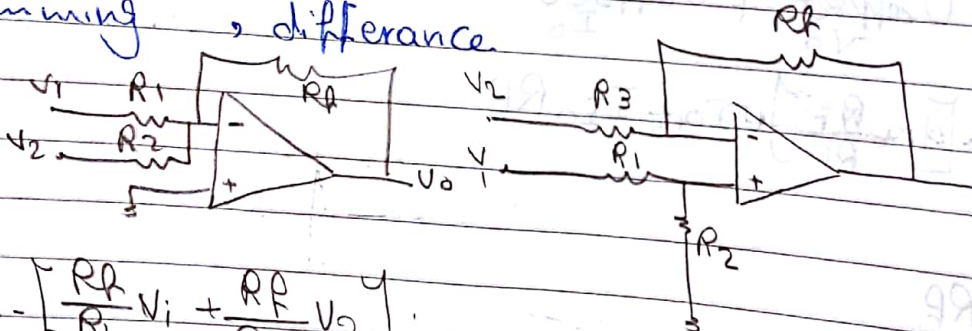


$$V_o = -\left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right]$$

$$V_o = V^+ \left[1 + \frac{R_f}{R_3}\right] - V_1 \frac{R_f}{R_1 + R_2} - V_2 \frac{R_f}{R_3}$$

④ integrator , differentiator



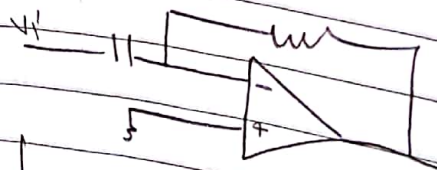
$$V_o = \int v_i(t) dt + V_o \times \frac{-1}{RC}$$




$$V_o = \frac{dv_i}{dt} \times -R_c$$


① ②

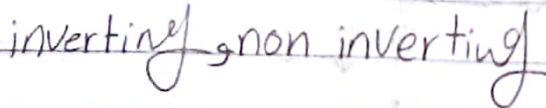

Amplifier 1593A


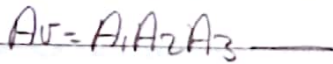


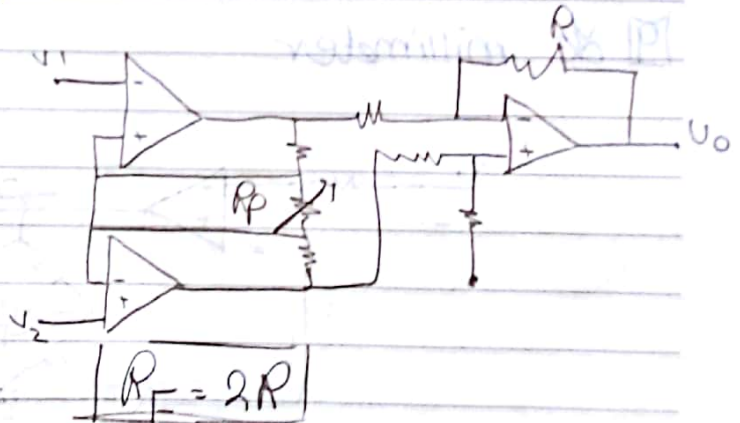يتم استنتاج ρ الدائرة للتحكم في V_1 و V_2
وبين التحكم في v_{load} عن طريق
المقاومة المتغيرة R_p




$$\frac{V_0}{V_1 - V_2} = \left[1 + \frac{2R}{R_P} \right]$$

Passive
R-L-C

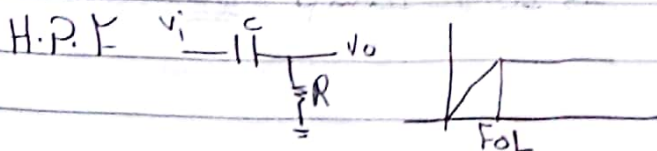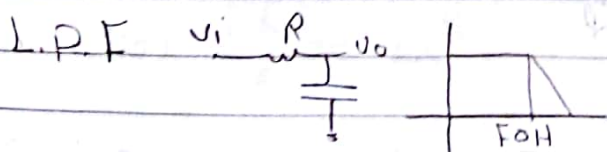

drive


1 op-amp-BJT

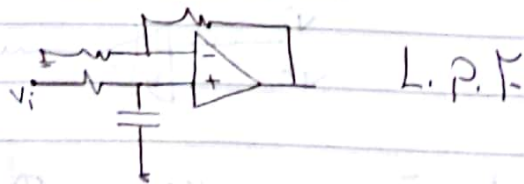

4 Unit

18] Dc millivoltmeter

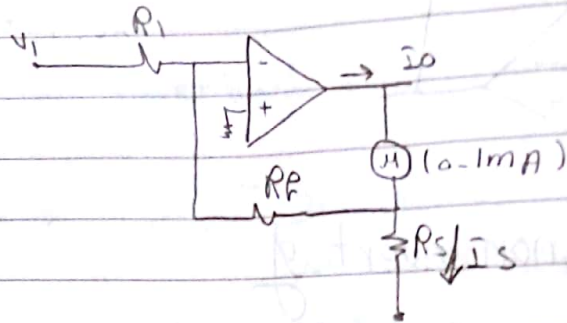- op-amp meter
- 1) $R_{in} \uparrow \uparrow$ $R_F \uparrow \uparrow$
 - 2) $\frac{I_s R_s}{I_0 R_s} = \frac{R_F}{R_i}$



$$V_o = -\frac{R_F}{R_i} V_i$$


$$\frac{I_s R_s}{I_0 R_s} = \frac{R_F}{R_i} V_i$$

$$\frac{I_o}{V_i} = \frac{R_F}{R_i R_s}$$


I_o و V_i قابل تنظیم است

19] Dc millimeter

V_{rms} میسازد

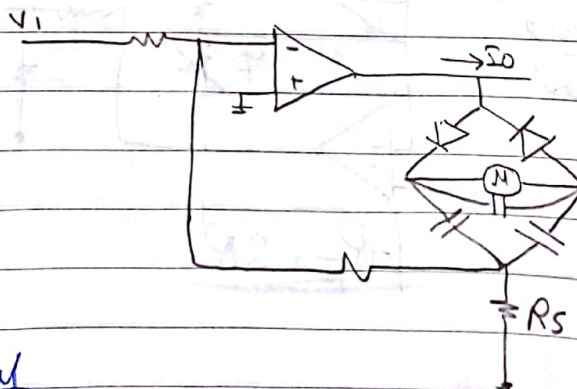

display
10] Driver

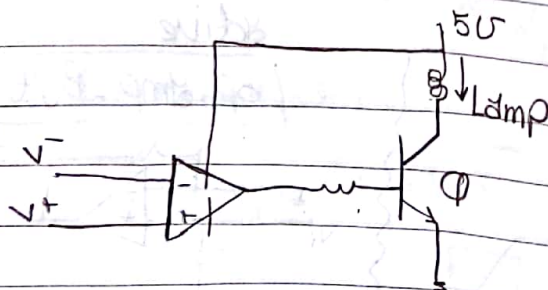

$V^+ > V^-$ $V_o +ve$ Φ on $\rightarrow I_c$ lamp on

$$\frac{1}{1 + \frac{R_F}{R_3}} = \frac{R_F}{R_3}$$

$$1 + \frac{R_F}{R_3}$$

$$V_O = V^+ - V^-$$

Date

Subject

[11] Controlled dependant source

حسب الدخل بيحكم خايجها كذا

$$I_O = I_1 = \frac{V_1}{R_1} = \left[\frac{1}{R_1} \right] V_1$$


← voltage control current source.

[3] Sheet


$$A_V = A_1 A_2 A_3$$

$$V_O = A_{VT} \cdot V_O$$


[4]

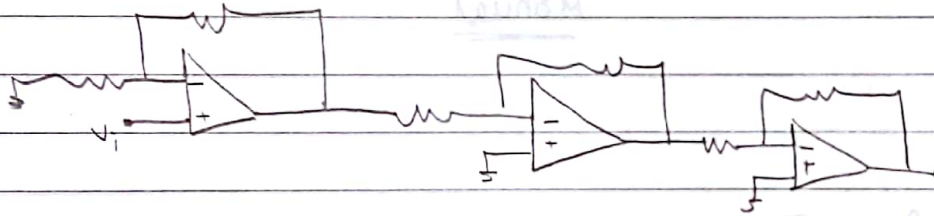

[5]

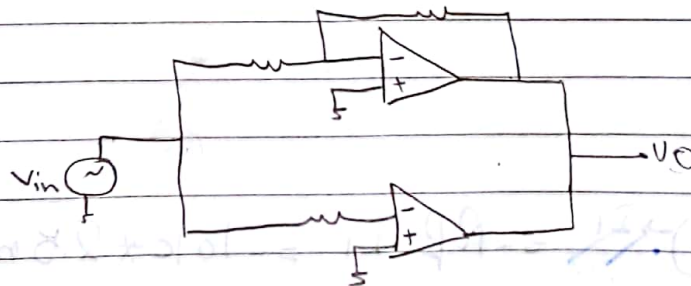

[6]

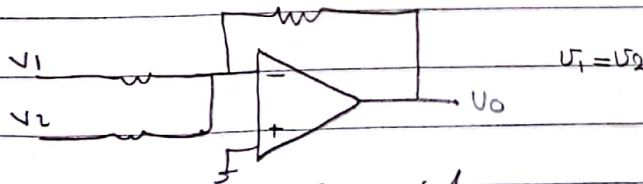

$$V_O = - \left[\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right]$$

$$[7] V_O = V_1^+ \left(1 + \frac{R_F}{R_3} \right) - V_2^- \left(-\frac{R_F}{R_3} \right)$$

$V_1^+ = \frac{R_1}{R_1 + R_2}$

Write